 


## Rrio\_requirements

\* dsauersanjose@aol.com 12/17/08

\* www.idea2ic.com



.OPTIONS method=gear GMIN=1e-18

VIN	INP	0	SIN(6	6	1K )
QP1	VP1	INP	VPNP	PNPL	1.04
QP2	VP2	OUT	VPNP	PNPL	1
QP3	VPNP	VP	VCC	PNPL	1
QP4	VP	VP	VCC	PNPL	1
RP1	VP1	0	5K		
RP2	VP2	0	5K		

QN1	VN1	INP	VNPN	NPNV	1.02
QN2	VN2	OUT	VNPN	NPNV	1
QN3	VNPN	VN	0	NPNV	1
QN4	VN	VN	0	NPNV	1

```

RN1      VCC     VN1      5K
RN2      VCC     VN2      5K
IBIAS    VIOUT   0        -.01u

VCC      VCC     0        12
VREF     VREF    0        6
IPNP     VP      0        20u
INPN     VCC     VN      20u

BDITA    VIOUT   0        I = ( V(VP2) - V(VP1) + V(VN2) - V(VN1) )/5000
BOTA     OUT     0        I = -1*( V(VIOUT) - V(VREF) )/5000
CCOMP    OUT     VIOUT  3p

.tran    1u      2m      0        1u

.model   NPNV npn BF=150
.model   PNPL pnp BF=150

.control
run
set      pensize = 2
*plot    v(out) v(inp)
dc       vin 0 12 100m
plot    v(out)-v(inp) title OffsetVoltageVsCommonMode
plot    v(vp1) v(vp2) v(vcc)-v(vn1) v(vcc)-v(vn2) title TailCurrentsVsCommonMode
alter   vcc dc = 1
dc       vin 0 1 1m
plot    v(out)-v(inp) title OffsetVoltageVsCommonMode
plot    v(vp1) v(vp2) v(vcc)-v(vn1) v(vcc)-v(vn2) title TailCurrentsVsCommonMode


.endc
.end


```


\* ======END=====

To Covert PDF to plain text click below  
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

 
**As time went on the supply voltage levels kept dropping which encouraged the development of Rail to Rail input and output Op Amps to be able to use all of the supply voltage range.**




 For the case of Bipolar transistors, this meant that two input stages need to be connected in parallel. Just doing so means most of the time both input stages are on and depending on which rail the inputs approach, one of the input stages will turn off.



 
In this simulation, a 1mV mismatch was introduced to the input pnps and a +.5mV mismatch was introduced to the npns. So for most of the common mode input range, there is a partial offset cancelation. At zero volts the npns are off and the pnp's offset dominates. At 12Volts the npn's dominate.



 



Another place to view things is the IR drop at the collector resistors for input transistors. If the resistors are small enough, the inputs can easily swing 200mV past both rails. This nodes later get fed into a dual input turn around circuit which converts the differential input signal from either input into a output current.

 The rail to rail feature sort of assumes that the supply voltage is high enough so that either input stage is on.



 On a 1volt supply, both pnp and npns are off at 500mV.  
Above and below this level will turn on one stage.



 

For a bipolar Rail To Rail Op Amp, this implies that there is a minimum supply voltage of two diodes and to sats in order that neither input stage is turned off.