Adding a piece wise linear noise source to a free running oscillator can show how the noise maps to jitter or PM or to a spectrum.

In this case a 2second/1kHz BW random PWL file is created.



Amplifier BAMP is clipping its output at +/- 10Volts.

Capacitor C1 is toggling between +/- 5volts. Noise source BPWL is messing up the timing. So in this case C1 has been adjusted to produce 40 whole cycles within 2 seconds.

Noise source BPWL is receiving a random 1VRMS signal with a bandwidth of 1KHz. This has been scaled down to +/- 100mV rms.



The Noise source BPWL can be seen on the inp input. But its PM effects are hard to see. A spectrum can show the details.

*=======	=Find Spect	rum=====							
linearize									
set	specwindow	= "nor	ne"						
spec	.5 1k	.5	v(out2	)					
plot	<pre>mag(out2)</pre>	loglog							
plot	mag(out2)	loglog	xlimit 1	0 100	ylimit	.001	100		
*=======	=Wrap_Up===								
.endc									
.end									
*									



The actual noise is appearing close to the peak signals at 20Hz and 60Hz and 100Hz, etc. Since white noise was applied, the slope of the adjacent noise sidebands around 20Hz drop in power to the  $1/f^2$  as they get farther away from 20Hz. The same is true for all the odd harmonics.

But it is also possible to get the same plot by doing a jitter plot on this oscillator, and then creating a PWL file which will be used to phase modulate a 20Hz signal. This will produce a spectrum which is very close.

And it is possible to map how the noise gets around to producing its sidebands at its magnitude and at its frequency.



*   * // \ F * C1 * C1 * C1 * C1		R2	co 2000 7/7 RO 1 OF							
· ///		~ ~ ~								
* * VpwlT OUT 0 PWL( + 0.0005 0.988835 +										
*========	Include	e_Noise_	File===							
.include	PWL_Fil	le.inc								
Rload	OUT	0	lk							
BAMP	OUT1	0	V =	9.9*tanh(	(V(INP)-V(INN))*10)					
RO	OUT1	OUT2	1							
CO	OUT2	0	500u							
Rl	VFB	0	1K							
R2	VFB	OUT2	1K							
R3	INN	OUT2	2.49K							
BPWL	INP	VFB	V =	.1*V(OUT)						
C1	INN	0	9.415u	IC= .1						
*========	Run_Sin	nulatior	J======							
*TRAN	TSTEP	TSTOP	TSTART	TMAX	20102					
.tran .control	5u	2	0	5u	UIC					
run										
set	pensize	e =	2							
plot	out2	inp	inn							
*========	Find Sp	pectrum=								
linearize										
set	specwir	ndow=	"none"							
spec	.5 1	lk	.5 1	(out2)						
plot	mag(out	t2) log	log							
plot	mag(out	t2) log	glog xli	imit 10 100	) ylimit .001 100					
.endc .end	•wrap_U <u>r</u>	p======								

2.18.10\_12.15PM dsauersanjose@aol.com Don Sauer http://www.idea2ic.com/