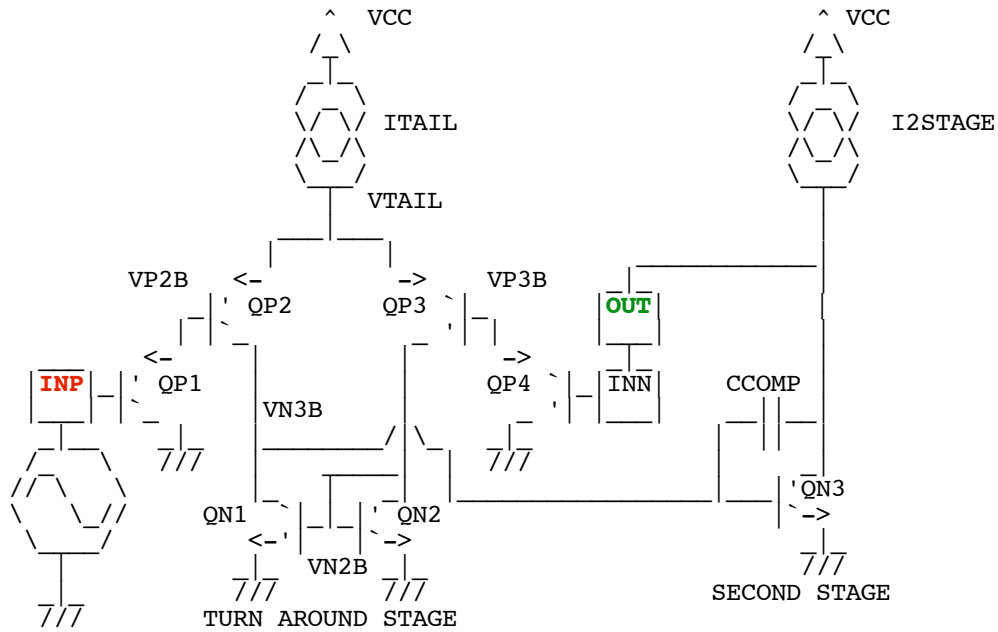


LM324_REQUIREMENTS

* dsauersanjose@aol.com 12/17/08
 * www.idea2ic.com



```
.OPTIONS method=gear GMIN=1e-18

VIN      INP    0      SIN(6  6.7      1K )
QP1      0      INP    VP2B    PNPL    1
QP2      VN3B   VP2B   VTAIL   PNPL    1
QP3      VN2B   VP3B   VTAIL   PNPL    1
QP4      0      OUT    VP3B    PNPL    1

QN1      VN3B   VN2B   0       NPNV   1
QN2      VN2B   VN2B   0       NPNV   1
QN3      OUT    VN3B   0       NPNV   1

VCC      VCC    0       12
ITAIL    VCC    VTAIL  50u
I2STAGE  VCC    OUT    100u

CCOMP    OUT    VN3B   20p

.tran    1u     2m     0       1u

.model   NPNV npn BF=150
.model   PNPL pnp BF=5
```

```
.control
run
set pensize = 2
plot v(inp) v(out)
```

```
.endc
.end
```


* =====END=====

To Covert PDF to plain text click below
<http://www.fileformat.info/convert/doc/pdf2txt.htm>

The LM324 is perhaps the best example of a product designed for the automotive market. At the time there was only a single 12volt supply available and hence the development of single supply Op Amps.

Its not that single supply Op Amps can't be used on Dual supplies or visa versa. The single supply title assumes certain input and output features.

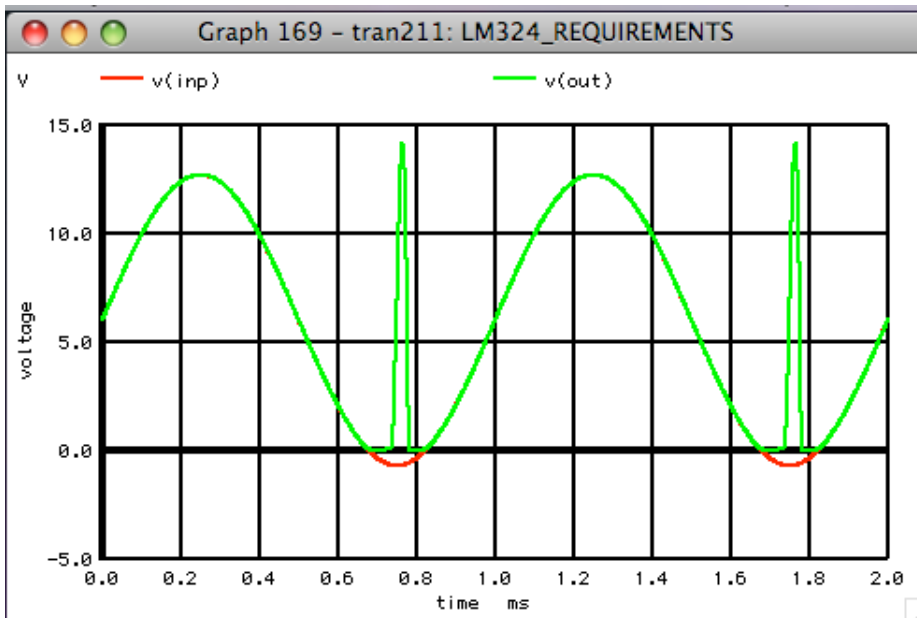For instance the LM324 input can function with both it inputs at the ground level on a single 12V supply. The LM741's inputs cannot do this. The automotive amplifiers were design to operate at a much lower supply voltage. In the case of the LM324, the output can swing to a saturation voltage above ground to give more output voltage swing.



This simulation shows some of the extra features that get designed within an Op Amp that may not appear in the data sheet. If care is not taken at the input stage, swinging a few hundred millivolts below ground can cause the output voltage swing to reverse phase.

