 


LC_transLine_1speed



www.idea2ic.com dsauersanjose@aol.com 4/15/08

```
.OPTIONS GMIN=1e-18 METHOD=euler ABSTOL=1e-18 TEMP=27 srcsteps = 1 gminsteps = 1
VIN      0      PWL( 0 0 2n 0 3.0n 1 18n 1 19.0n 0)
RIN      VIN    1      50
C1       VIN    0      1.6p
XLC1     1      2      LC1
XLC2     2      3      LC1
XLC3     3      4      LC1
XLC4     4      5      LC1
XLC5     5      6      LC1
XLC6     6      7      LC1
XLC7     7      8      LC1
XLC8     8      9      LC1
XLC9     9      10     LC1
XLC10    10     OUT    LC1
C2       OUT    0      -1.6p
```

```
ROUT     OUT    0      50
C3       OUT    0      10f
.tran    0.01n 30n 0 30n
```

.control

***#1===First_Test_Reflection_at_50_Ohms=====**

run

plot v(1) v(6) out title RC_160ps_1GHz_50out

***#2===First_Test_Reflection_at_100_Ohms=====**

alter ROUT resistance = 100

run

plot v(1) v(6) out title RC_160ps_1GHz_100out

***#3===First_Test_Reflection_at_20_Ohms=====**

alter ROUT resistance = 20

run


plot v(1) v(6) out title RC_160ps_1GHz_20out

.endc

.SUBCKT LC1 IN OUT

```
L1      IN      OUT    8n
C1      OUT    0      3.2p
.ENDS   LC1
```

.SUBCKT LC1 IN OUT

 

8nH_3.2pF =>50ohms @ 1Ghz 50*3.2p =160ps

*** http://www.idea2ic.com/PlayWithJavascript/L_C_R_F.html**

.end


=====END_OF_SPICE=====

***#1===First_Test_Reflection_at_50_Ohms=====**

Capacitors C1 and C2 are added such that each inductor see 1.6pF on each of its sides. The subcircuit is modeled as a simple LC


for simplicity sake.

 Thinking in terms of 50 Ohms and 3.2ps,
the total delay is 10 time constants
of 160ps which is 1.6nsec.



*#2===First_Test_Reflection_at_100_Ohms=====

 Not terminating with 50 ohms has expected results.



The voltage divider effect for any voltage
has a effective $10 \times (50 \text{ Ohms}) (3.2 \text{ pF})$ delay
from the output reflected back to the input.

*#3===First_Test_Reflection_at_20_Ohms=====

