


*=====Better_Bessel_GroupDelay=====

The dissection of the harmonics of a lowpass filter's output can show how phase delay effects group delay.

Below is a behavioral model for a 6 pole Bessel filter.

=====
Better_Bessel_6P_State_Variable

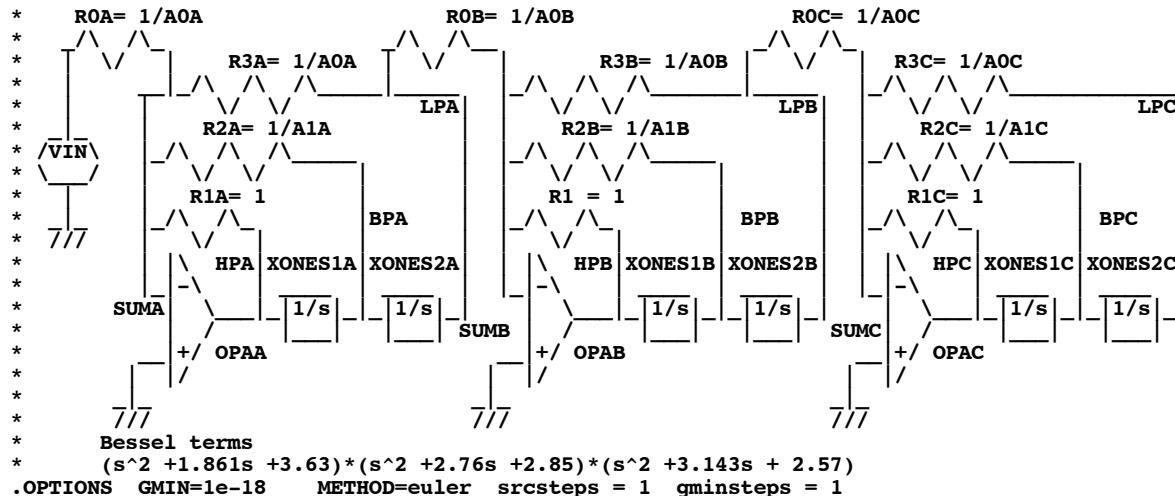* dsauersan jose@aol.com
* www.idea2ic.com
* 8.13.10_10.02AM




*=====Using_Simple_Amplifiers=====

Pretty idealized models are being used for Op Amps and integrators.

*V_PULSE#	NODE_P	NODE_N	DC	VALUE	PULSE (VINIT	VPULSE	TDELAY	TRISE	TFALL	WIDTH	PERIOD)
V_IN	VIN	0	DC	0	PULSE (-1	1	100u	100u	100u	1	2) AC = 1
ROA	VIN	SUMA	.333									
R1A	SUMA	HPA	1									
R2A	SUMA	BPA	.54									
R3A	SUMA	LPA	.333									
BOPA1A	HPA	0	V =	5*tanh(tanh((-v(SUMA))*100)*100)								
XONES1A	HPA	BPA	ONE_S									
XONES2A	BPA	LPA	ONE_S									
ROB	LPA	SUMB	.35									
R1B	SUMB	HPB	1									
R2B	SUMB	BPB	.362									
R3B	SUMB	LPB	.35									
BOPA1B	HPB	0	V =	5*tanh(tanh((-v(SUMB))*100)*100)								
XONES1B	HPB	BPB	ONE_S									
XONES2B	BPB	LPB	ONE_S									
ROC	LPB	SUMC	.389									
R1C	SUMC	HPC	1									
R2C	SUMC	BPC	.318									
R3C	SUMC	LPC	.389									
BOPA1C	HPC	0	V =	5*tanh(tanh((-v(SUMC))*100)*100)								
XONES1C	HPC	BPC	ONE_S									
XONES2C	BPC	LPC	ONE_S									
BinV	LPD	0	V =	-V(LPC)								

=====
Integrator_Cell

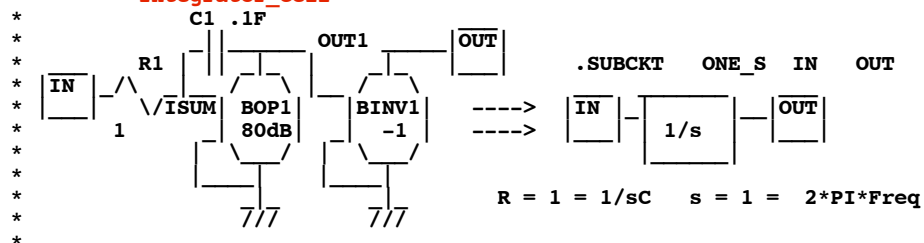

```

.SUBCKT      ONE_S      IN      OUT
R1          IN      ISUM      1
C1          ISUM      OUT1      .1
BOP1       OUT1      0      V =      5*tanh(tanh((-v(ISUM))*100)*100)
BINV1      OUT      0      V =      -v(OUT1)
.ends

```



***=====Simple_Simulations=====**

It is not hard to do AC and Transient tests.

```

=====
.control
ac          dec      500      .01      100
plot       db(lpc)
*TRAN      TSTEP    TSTOP    TSTART   TMAX
tran       50m      7.95     4        50m

```

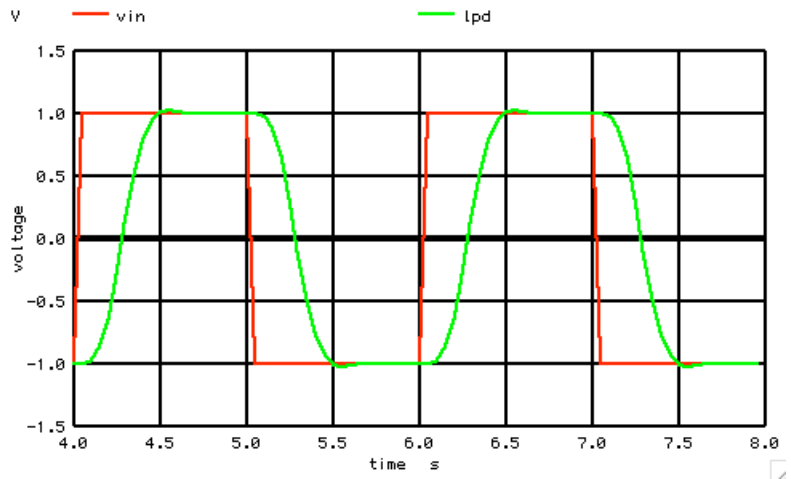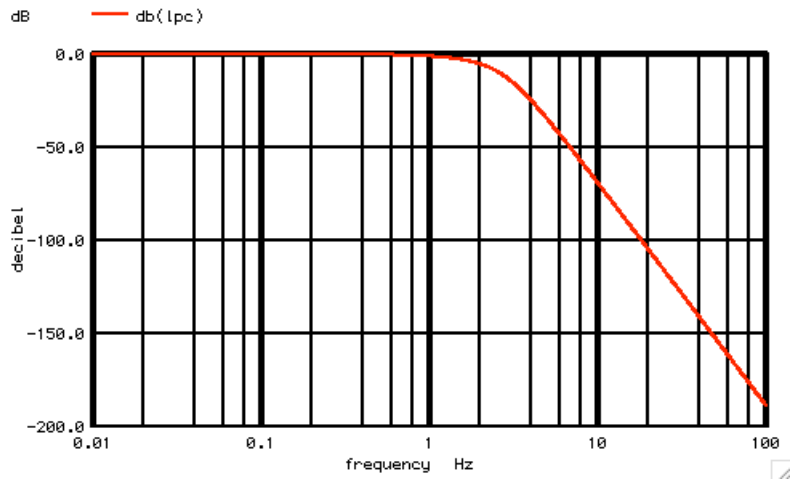


While the roll off of a Bessel is not as sharp as a Butterworth, there is no ringing at the output. It is like the output is just a time shifted input with its corners rounded off.

***=====Look_at_the_Output_Spectrum=====**

The FFT reveals that the fundamental and third and

fifth harmonic got through the lowpass filter. So the
bessel is not as sharp as a butterworth.
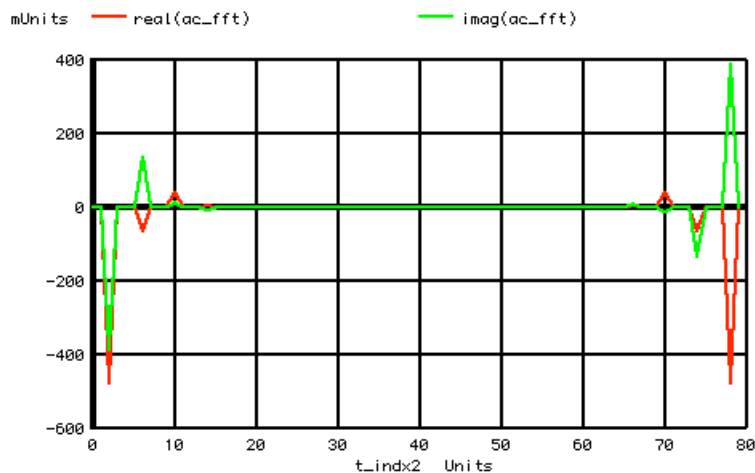
```
=====
llinearize
plot      vin      lpd
let      numb2    = length(vin)
print    numb2
let      t_indx2  = vector($&numb2)
let      ac       = lpd +j(0)
let      ac_fft   = fft(ac)
plot     real(ac_fft) imag(ac_fft) vs t_indx2
```




*=====The_Harmonics_Can_Be_Dissected=====

The dissection of the harmonics shows why there is
no ringing.

```
=====
let      funbin = 2
let      unvect      = unitvec($&numb2)
let      fundspec    = unvect*0 +j(0)
let      fundspec[2] = real(ac_fft[2])      +j(imag(ac_fft[2] ))
let      fundspec[numb2-2] = real(ac_fft[numb2-2]) +j(imag(ac_fft[numb2-2] ))
let      fund        = ifft(fundspec)
let      thirdspect  = unvect*0 +j(0)
let      thirdspect[6] = real(ac_fft[6])      +j(imag(ac_fft[6] ))
let      thirdspect[numb2-6] = real(ac_fft[numb2-6]) +j(imag(ac_fft[numb2-6] ))
let      third       = ifft(thirdspect)
let      fifthspect  = unvect*0 +j(0)
let      fifthspect[10] = real(ac_fft[10])     +j(imag(ac_fft[10] ))
let      fifthspect[numb2-10] = real(ac_fft[numb2-10]) +j(imag(ac_fft[numb2-10] ))
let      fifth       = ifft(fifthspect)
let      seventhspec = unvect*0 +j(0)
let      seventhspec[14] = real(ac_fft[14])    +j(imag(ac_fft[14] ))
let      seventhspec[numb2-14] = real(ac_fft[numb2-14]) +j(imag(ac_fft[numb2-14] ))
let      seventh     = ifft(seventhspec)
let      sum         = fund + third + fifth + seventh
set      scale time
plot     fund third fifth seventh sum

plot     fund third fifth seventh sum xlimit 5.2 5.7
.endc
```

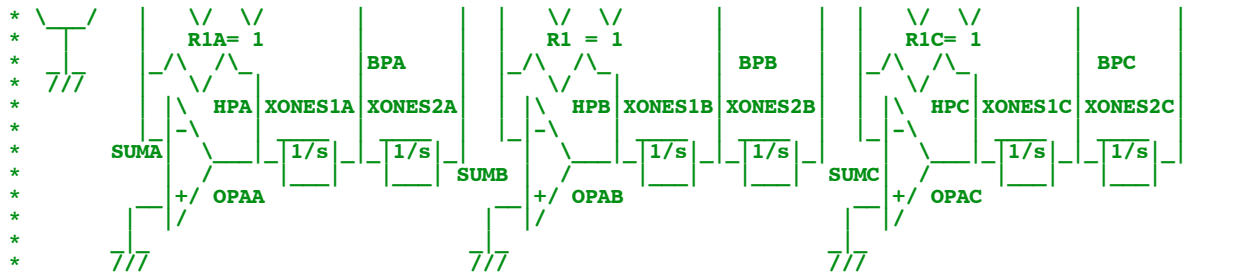
Butterworth terms

$$(s^2 + 0.5176s + 1)(s^2 + 1.4142s + 1)(s^2 + 1.9319s + 1)$$

.OPTIONS GMIN=1e-18 METHOD=euler srcsteps = 1 gminsteps = 1

*V_PULSE#	NODE_P	NODE_N	DC	VALUE	PULSE(VINIT	VPULSE	TDELAY	TRISE	TFALL	PWIDTH	PERIOD)
V_IN	VIN	0	DC	0	PULSE(-1	1	100u	100u	100u	1	2) AC = 1
R0A	VIN	SUMA	1									
R1A	SUMA	HPA	1									
R2A	SUMA	BPA	1.9319									
R3A	SUMA	LPA	1									
BOPA1A	HPA	0	V =	5*tanh(tanh((-v(SUMA))*100)*100)								
XONES1A	HPA	BPA	ONE_S									
XONES2A	BPA	LPA	ONE_S									
ROB	LPA	SUMB	1									
R1B	SUMB	HPB	1									
R2B	SUMB	BPB	.707									
R3B	SUMB	LPB	1									
BOPA1B	HPB	0	V =	5*tanh(tanh((-v(SUMB))*100)*100)								
XONES1B	HPB	BPB	ONE_S									
XONES2B	BPB	LPB	ONE_S									
ROC	LPB	SUMC	1									
R1C	SUMC	HPC	1									
R2C	SUMC	BPC	.5176									
R3C	SUMC	LPC	1									
BOPA1C	HPC	0	V =	5*tanh(tanh((-v(SUMC))*100)*100)								
XONES1C	HPC	BPC	ONE_S									
XONES2C	BPC	LPC	ONE_S									
BinV	LPD	0	V =	-V(LPC)								

=====Integrator_Cell=====

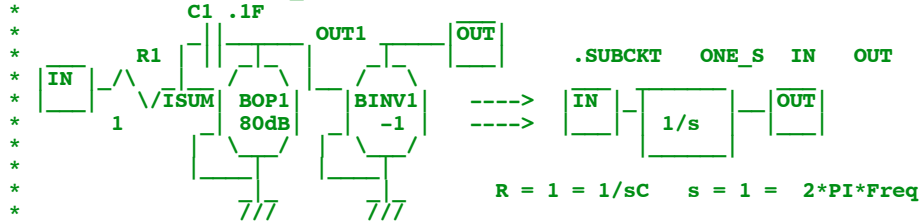

.SUBCKT	ONE_S	IN	OUT
R1	IN	ISUM	1
C1	ISUM	OUT1	.1
BOP1	OUT1	0	V = 5*tanh(tanh((-v(ISUM))*100)*100)
BINV1	OUT	0	V = -v(OUT1)

=====A_Bessel_is_Best_for_Low_Phase_Distortion=====

```
.control
ac dec 500 .01 100
plot db(lpc)
*TRAN TSTEP TSTOP TSTART TMAX
tran 50m 7.95 4 50m
```

```
linearize
plot vin lpd
let numb2 = length(vin)
print numb2
let t_indx2 = vector($&numb2)
let ac = lpd +j(0)
let ac_fft = fft(ac)
plot real(ac_fft) imag(ac_fft) vs t_indx2

let funbin = 2
let unvect = unitvec($&numb2)
let fundspec = unvect*0 +j(0)
let fundspec[2] = real(ac_fft[2]) +j(imag(ac_fft[2] ))
let fundspec[numb2-2] = real(ac_fft[numb2-2]) +j(imag(ac_fft[numb2-2] ))
```

```

let      fund                =  ifft(fundspec)
let      thirdspeak         =  unvect*0 +j(0)
let      thirdspeak[6]     =  real(ac_fft[6])      +j(imag(ac_fft[6] ))
let      thirdspeak[numb2-6] =  real(ac_fft[numb2-6]) +j(imag(ac_fft[numb2-6] ))
let      third              =  ifft(thirdspeak)
let      fifthspeak        =  unvect*0 +j(0)
let      fifthspeak[10]    =  real(ac_fft[10])     +j(imag(ac_fft[10] ))
let      fifthspeak[numb2-10] =  real(ac_fft[numb2-10]) +j(imag(ac_fft[numb2-10] ))
let      fifth             =  ifft(fifthspeak)
let      seventhspeak     =  unvect*0 +j(0)
let      seventhspeak[14]  =  real(ac_fft[14])     +j(imag(ac_fft[14] ))
let      seventhspeak[numb2-14] =  real(ac_fft[numb2-14]) +j(imag(ac_fft[numb2-14] ))
let      seventh          =  ifft(seventhspeak)
let      sum = fund + third + fifth + seventh
set      scale  time
plot     fund  third  fifth  seventh  sum

plot     fund  third  fifth  seventh  sum xlimit 5.2 5.7
.endc

.end

```