

Bessel_6P_Group_Delay

```
.OPTIONS GMIN=1e-18 METHOD=euler srcsteps = 1 gminsteps = 1
*=====
VREF      VREF      0      PULSE( -.5 .5 1u 1u 1u 10m 20m )
.include Bessel_6P_VCF_1.txt
.include Bessel_6P_VCF_100m.txt
.include Bessel_6P_VCF_30m.txt
Vtime     Vtime     0      PWL ( 0 0 40m 12.566370614359172)
BIN       VIN       0      v=    v(VA)*v(OUTA) + v(VB)*v(OUTB) + v(VC)*v(OUTC)
B1       OUT1      0      v=    v(V1S)*sin(1*v(Vtime))+ v(V1C)*cos(1*v(Vtime))
B3       OUT3      0      v=    v(V3S)*sin(3*v(Vtime))+ v(V3C)*cos(3*v(Vtime))
B5       OUT5      0      v=    v(V5S)*sin(5*v(Vtime))+ v(V5C)*cos(5*v(Vtime))
B7       OUT7      0      v=    v(V7S)*sin(7*v(Vtime))+ v(V7C)*cos(7*v(Vtime))
B9       OUT9      0      v=    v(V9S)*sin(9*v(Vtime))+ v(V9C)*cos(9*v(Vtime))
B11      OUT11     0      v=    v(V11S)*sin(11*v(Vtime))+ v(V11C)*cos(11*v(Vtime))
BALL     OUTALL    0      v=    v(OUT1)+ v(OUT3)+ v(OUT5)+ v(OUT7) +v(OUT9) +v(OUT11)
V1S      V1S      0      DC    .5
V1C      V1C      0      DC    .5
V3S      V3S      0      DC    .5
V3C      V3C      0      DC    .5
V5S      V5S      0      DC    .5
V5C      V5C      0      DC    .5
V7S      V7S      0      DC    .5
V7C      V7C      0      DC    .5
V9S      V9S      0      DC    .5
V9C      V9C      0      DC    .5
V11S     V11S     0      DC    .5
V11C     V11C     0      DC    .5

VA       VA       0      DC    1
VB       VB       0      DC    0
VC       VC       0      DC    0

.control
set      pensize = 2
foreach PWLNumb 0 1 2
if      ($PWLNumb = 0)
alter   va dc = 1
endif
if      ($PWLNumb = 1)
alter   va dc = 0
alter   vb dc = 1
endif
if      ($PWLNumb = 2)
alter   vb dc = 0
alter   vc dc = 1
endif

tran     .05m     40m     0     .05m
linearize
set      specwindow = "rectangular"
spec     25      1000    25      v(vin)


set      s1= im(vin[1])
set      c1= real(vin[1])
set      s3= im(vin[5])
set      c3= real(vin[5])
set      s5= im(vin[9])
set      c5= real(vin[9])
set      s7= im(vin[13])
set      c7= real(vin[13])
set      s9= im(vin[17])
set      c9= real(vin[17])
set      s11= im(vin[21])
set      c11= real(vin[21])
alter    v1s dc = $s1
alter    v1c dc = $c1
alter    v3s dc = $s3
alter    v3c dc = $c3
alter    v5s dc = $s5
alter    v5c dc = $c5
alter    v7s dc = $s7
alter    v7c dc = $c7
alter    v9s dc = $s9
alter    v9c dc = $c9
alter    v11s dc = $s11
alter    v11c dc = $c11
tran     .05m     40m     0     .05m
plot     vin     out1 out3 out5 out7 out9 out11 outall 1.1*vref
plot     vin     out1 out3 out5 out7 out9 out11 outall 1.1*vref xlimit 20m 24m
```

```
end
.endc
.end
```


=====END_OF_SPICE=====

A good way to see how the Bessel provides for Low Phase Distortion is to view what is happening to a input square wave's harmonics in a bessel filter.

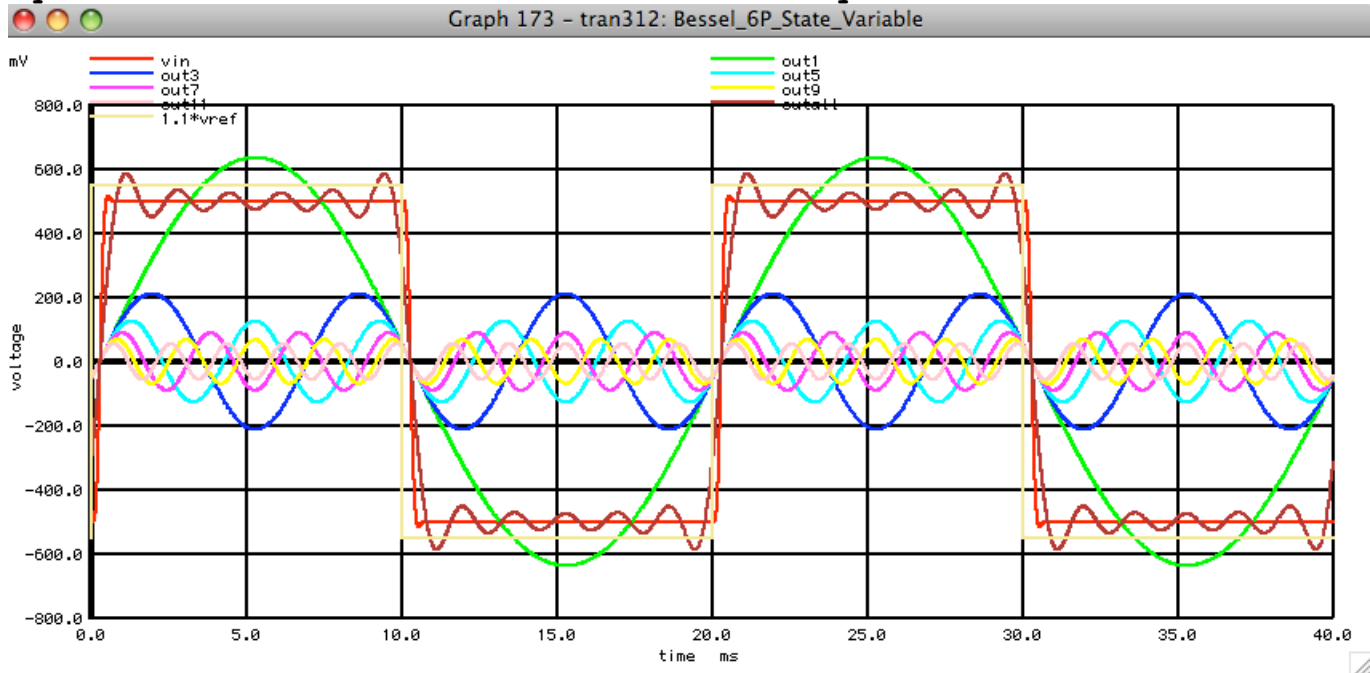
The vin signals for the graph below come from the Voltage Controlled filter simulations. This signal's odd harmonics are plotted up to the 11th harmonic. The fundamental and these harmonics are then summed together to provide a outall signal. The reference square wave that went into the VCF is shown in yellow.



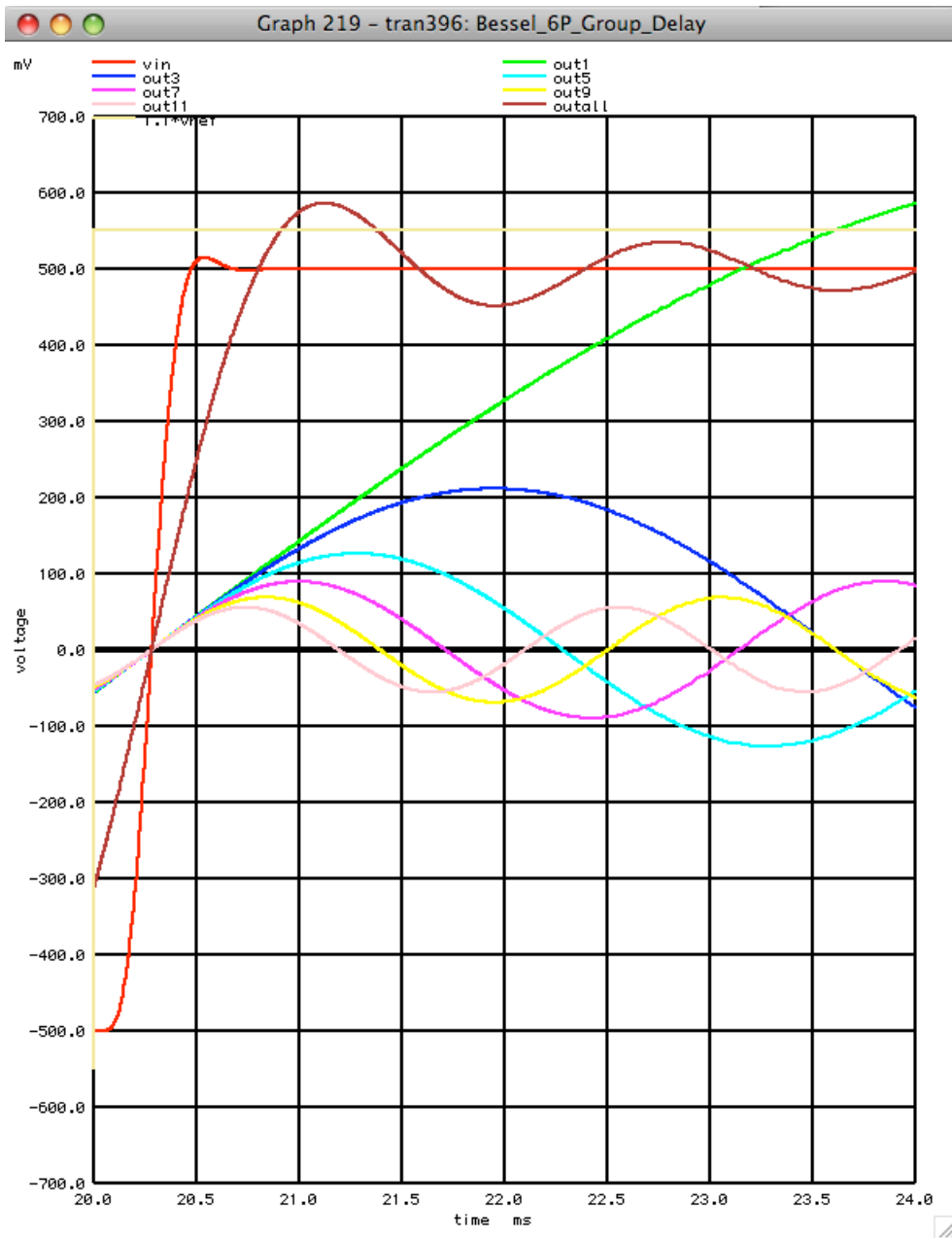
Obviously 11 harmonics are not enough to reconstruct the vin signal. In this case the 3dB bandwidth was at the 40th harmonic. The delay of vin and all its harmonics needs to be looked at with higher resolution.



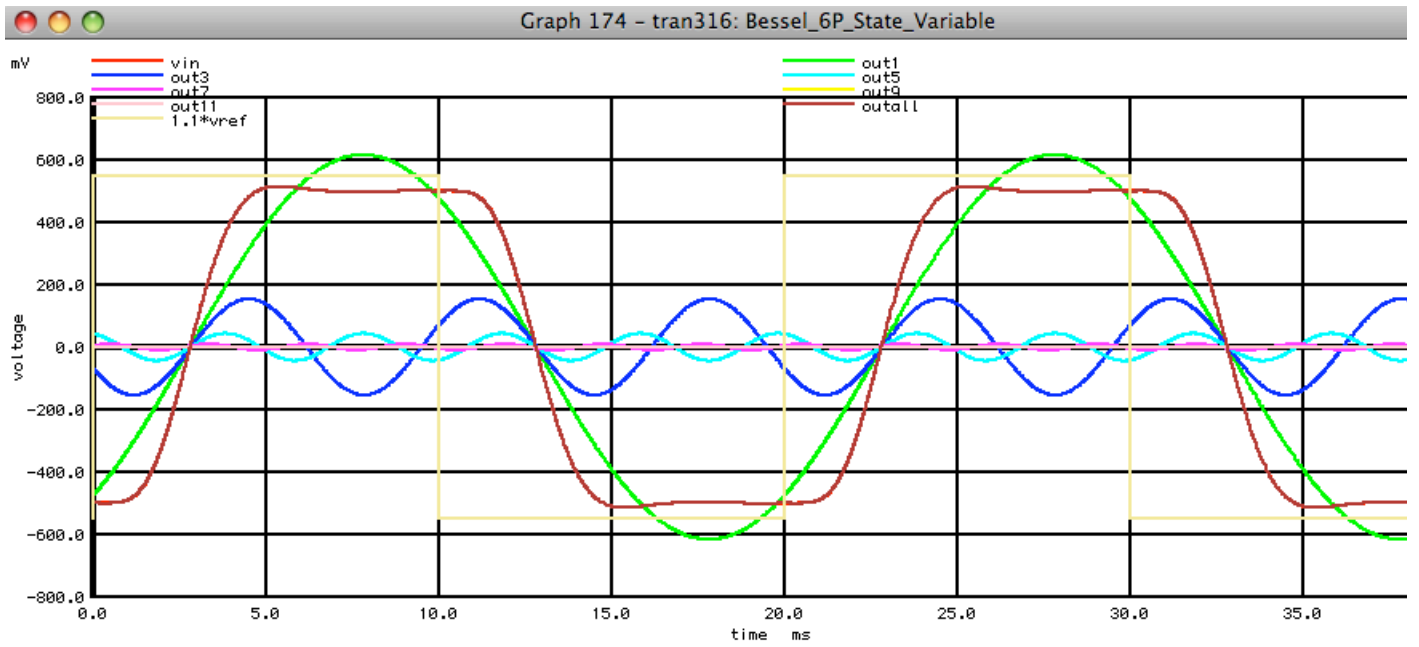All components of the vin signal are time delayed from the reference signal by the same 300usec.



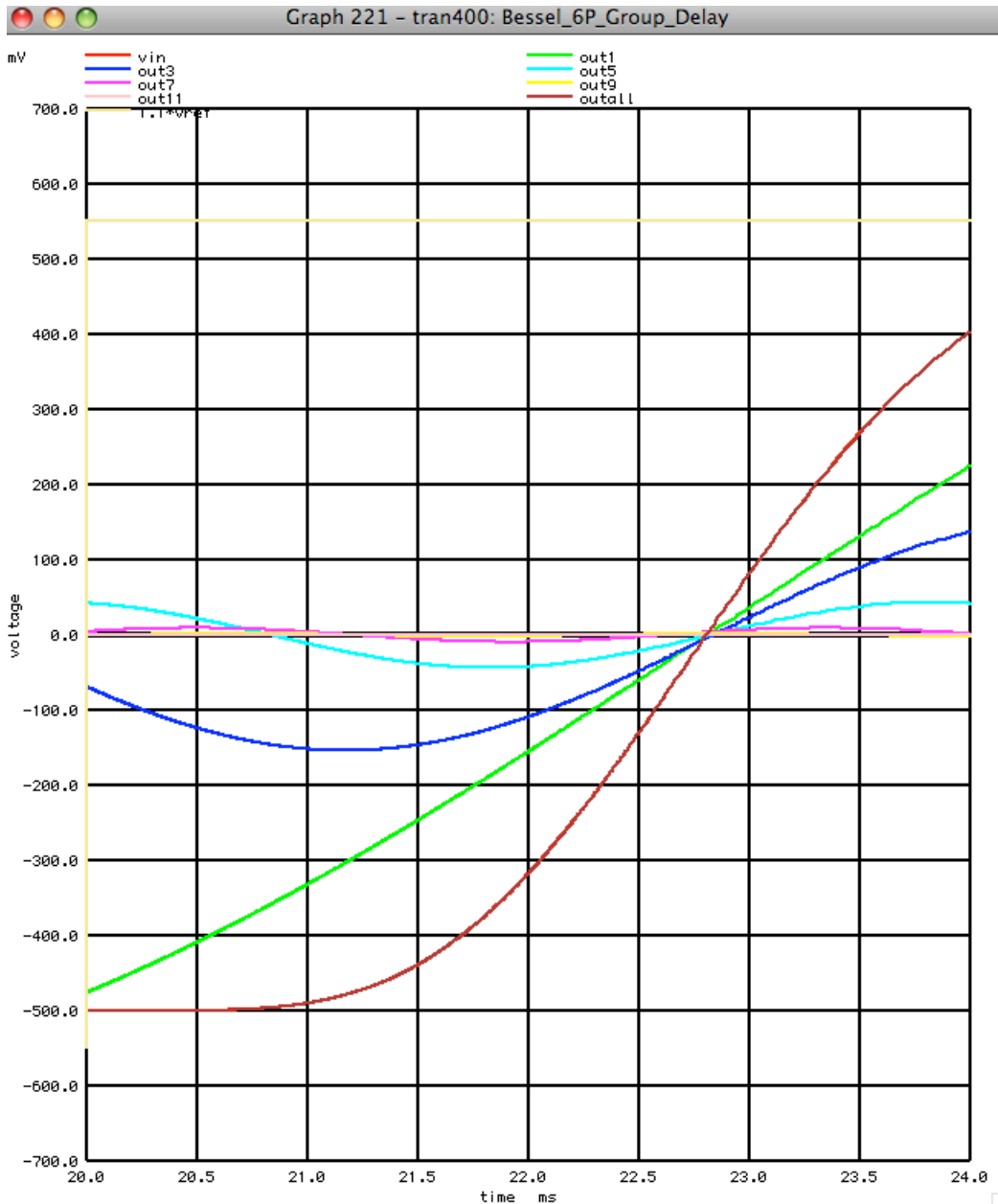When the Bessel's frequency response is reduced by a factor of ten, there is now about a 2.7msec delay in all components of v_{in} . Only the third and fifth harmonics are now present.



Finer resolution reveals that the fundamental and all it's harmonics are being shifted by the same 2.7msec time delay. Hence the phase relationship between the fundamental and all it's harmonics is conserved without any phase distortion. Another term is group delay which can be seen that the whole signal as group of frequencies have be delayed by the same amount. This does not apply to a butterworth filter.