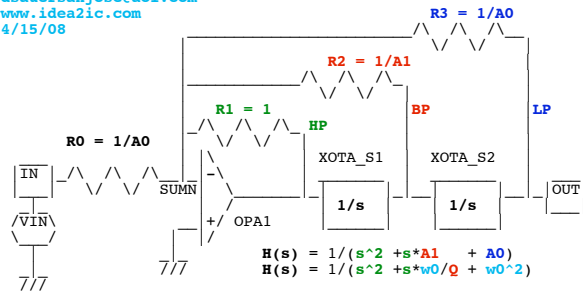


State_Variable_OTA_1KHz

* dsauersanjose@aol.com
 * www.idea2ic.com
 * 4/15/08



$$H(s) = 1/(s^2 + s*A1 + A0)$$


$$H(s) = 1/(s^2 + s*w0/Q + w0^2)$$

Set **A0 = 1** and scale **s** to 1KHz
 Then **R2 = Q** and **s = 2*PI*1KHz**

```
.OPTIONS GMIN=1e-12 METHOD=trap srcsteps = 1 gminsteps = 1
=====
V_IN VIN 0 AC 1 DC 0
R0 VIN SUMN 10k
R1 SUMN HP 10k
R2 SUMN BP 100k
R3 SUMN LP 10k
XOPA1 SUMN 0 HP OPA
XOTAS1 HP BP OTA_S
XOTAS2 BP LP OTA_S
.ac dec 50 10k
```

==OTAs Can Perform The Exact Same Function==
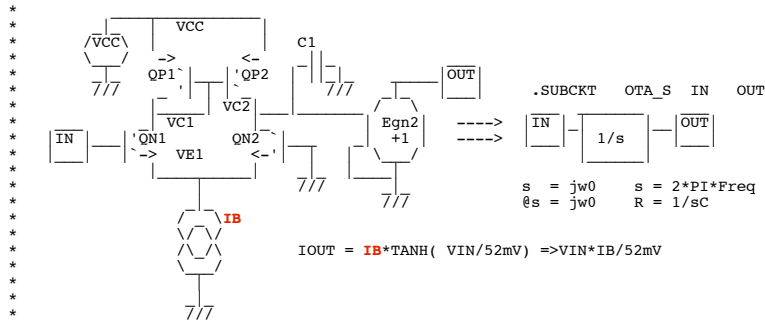
```
.control
run
plot db(bp) db(hp) db(lp) title StateVariable_Q_10
==Q Is Still Defined By FeedBack=====
alter R2 resistance = 10k
run
plot db(bp) db(hp) db(lp) title StateVariable_Q_1
.endc
```




$$s = jw0 \quad s = 2*PI*Freq$$

$$\hat{s} = jw0 \quad R = 1/sC$$

$$I_{OUT} = I_B * \tanh(VIN/52mV) \Rightarrow VIN * I_B / 52mV$$

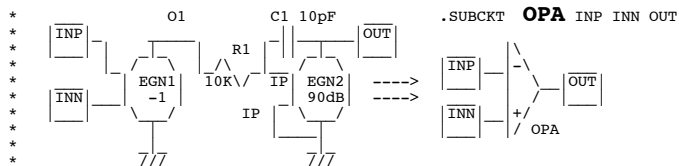http://www.idea2ic.com/PlayWithJavascript/R_C_Freq.html



```

.SUBCKT OPA INP INN OUT
EGN1 01 0 INP INN -1
EGN2 02 0 IP 0 -1000000
R1 01 01 IP 10k
C1 02 02 IP 10p

```

.ends

```

.SUBCKT OTA_S IN OUT
QN1 VC1 IN VE1 NPNP
QN2 VC2 0 VE1 NPNP
QP1 VC1 VC1 VCC PNPP
QP2 VC2 VC1 VCC PNPP
IB VE1 0 5.2u
VCC VCC 0 DC 2
EGN2 02 0 VC2 0 +1
C1 VC2 0 .01592u

```

.ends

```

.model NPNP NPN( BF=2100 VAF=216 )

```

```


.model PNPP PNP( BF=2100 VAF=210 )

```

.end

=====END_OF_SPICE=====

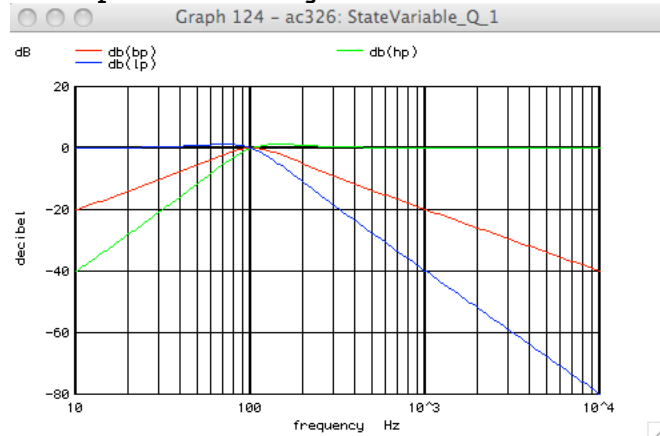A real OTA and capacitor with a voltage buffer can replace the integrator with no effect



Now R1->R3 independently controls Q
The frequency however now is independently control by bias current IB of the OTA.

Graph 121 - ac323: StateVariable_Q_10

