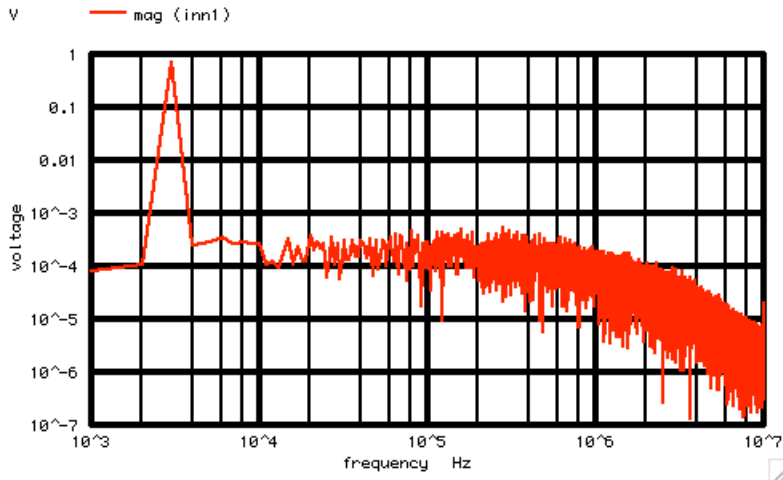
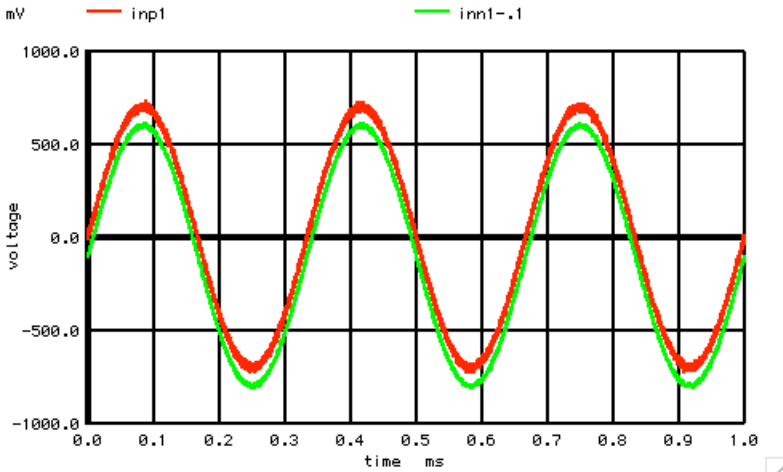


The output of the comparator is being latched at a 20MHz rate. This simulation is using a simple sample and hold.



The spectrum of the capacitor voltage will have a slightly lower bandwidth. At lower frequencies, the capacitor will track the input signal, noise and all.



The voltage across the capacitor shows what the a UP/Down counter running off the same latch digital output should be seeing.

There appears to be less noise in the capacitor, since the comparator was not simulated with infinite gain bandwidth.


```

*plot          inpl out1 inn1 out0
plot          out1 inn1
plot          out0 out1/1.1 5*cntl xlimit .5m .502m

echo          "=====FFT_and_Plot======"
linearize
let          FFT_BandWidth_Hz =      10Meg
let          FFT_resolution_Hz =     1k
echo          "FFT_BandWidth_Hz=     $&FFT_BandWidth_Hz"
echo          "FFT_resolution_Hz=    $&FFT_resolution_Hz"
set          specwindow=            "rectangular"
spec         $&FFT_resolution_Hz    $&FFT_BandWidth_Hz    $&FFT_resolution_Hz    v(inn1)
let expect_V = (sqrt(2)/sqrt(500k/1k))/(1+(frequency/550k)*(frequency/500k)*(frequency/500k)*(frequency/500k)*(frequency/500k))
plot         mag (inn1) loglog

destroy
destroy

echo          "=====FFT_and_Plot======"
linearize
let          FFT_BandWidth_Hz =      10Meg
let          FFT_resolution_Hz =     1k
echo          "FFT_BandWidth_Hz=     $&FFT_BandWidth_Hz"
echo          "FFT_resolution_Hz=    $&FFT_resolution_Hz"
set          specwindow=            "rectangular"
spec         $&FFT_resolution_Hz    $&FFT_BandWidth_Hz    $&FFT_resolution_Hz    v(inpl)
let expect_V = (sqrt(2)/sqrt(500k/1k))/(1+(frequency/550k)*(frequency/500k)*(frequency/500k)*(frequency/500k)*(frequency/500k))
plot         mag (inpl) loglog
echo          "=====done======"

.endc
.end

```

7.22.11_12.49PM
dsauersanjose@aol.com
Don Sauer