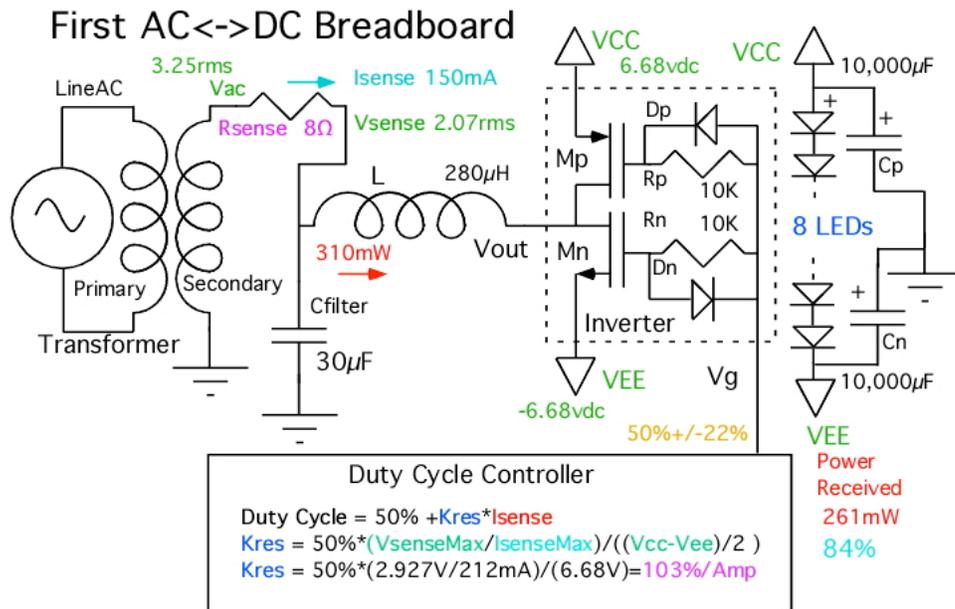



A RECTIFIER LESS AC<=>DC CONVERTER

12/945,704 filed 011-12-2010





A Rectifier-less Bidirectional AC to DC converter is just a simple DC to DC being used differently. The duty cycle of a DC to DC converter defines an output voltage. If this output node instead gets connected across a secondary of an AC transformer, and if the duty cycle gets defined to track secondary current, then the secondary will be seeing a simulated resistor across it. This simulated resistor will absorb energy and transfer it to the split supplies. It is based on using the [Energy Harvesting Resistor](#) described here.

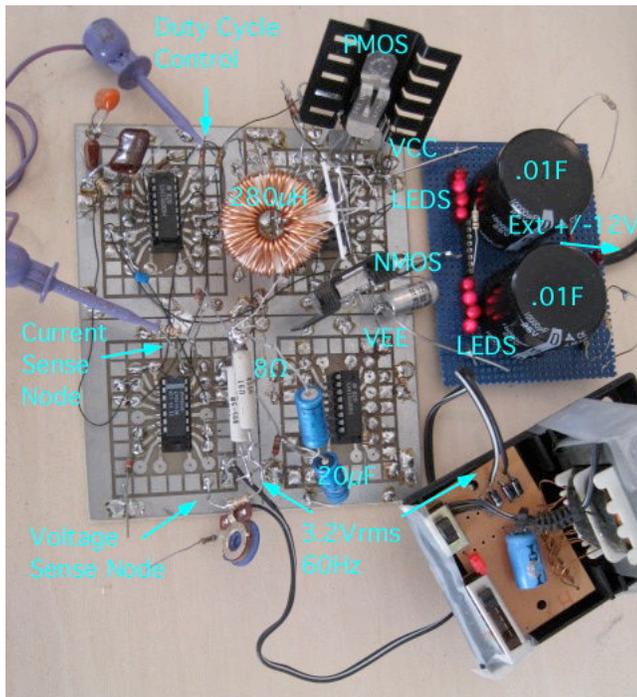The circuit and equations are shown above. The working breadboard is shown below.





This breadboard takes a 3.2Volt rms 60 Hz input directly off a secondary of an ac line transformer, and transforms it directly into +/- 6.7 Volt splits supplies to drive 8 LEDs. Most of the circuit is for duty cycle modulation experiments.

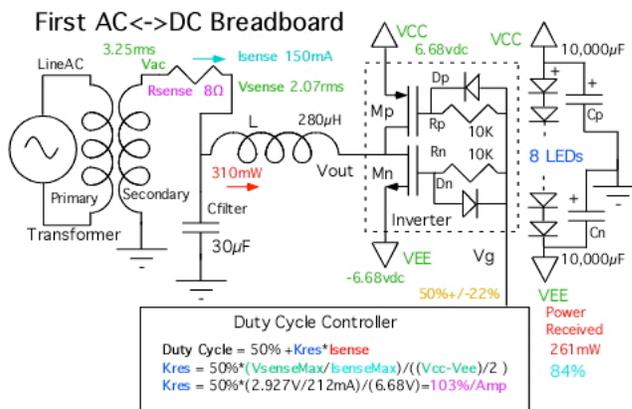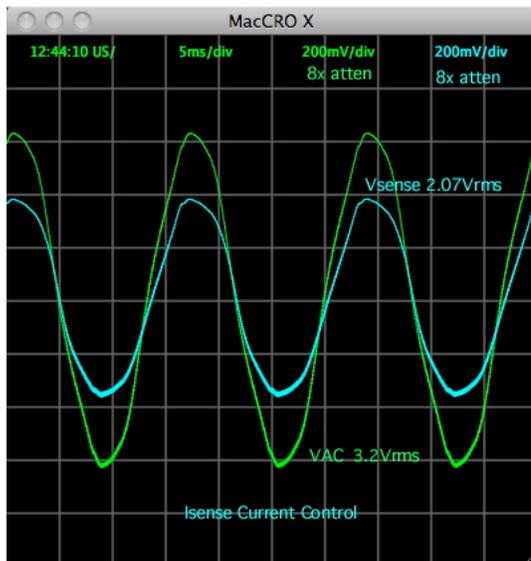And this is all being done using analog circuitry. The full schematic is included at the end. Everything appears to be working as expected.





There appears to be two main modes of operation. The first mode is to measure the **secondary current**, and then use it to modulate the duty cycle of a simple DC to DC converter above and below 50%. In the breadboard, this causes the secondary to think it is seeing a 22 Ohm resistor across it. The modulating duty cycle is multiplexing the **150mA rms input** current to the two supplies. The actual AC waveforms of the secondary voltage **Vac** and the **Vsense** voltage are shown above. Both waveforms are on the same scale. The current flowing across the 8 Ohm sense resistor is the secondary current.

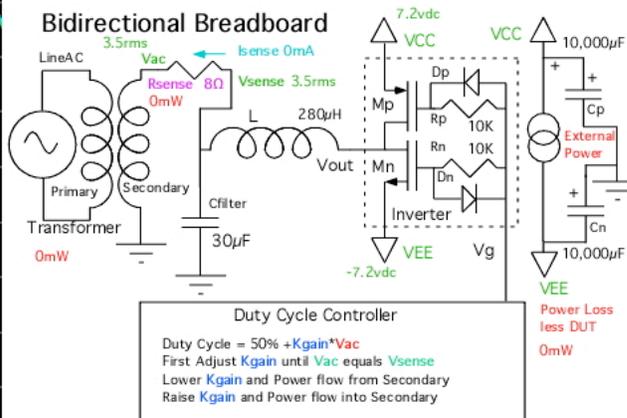
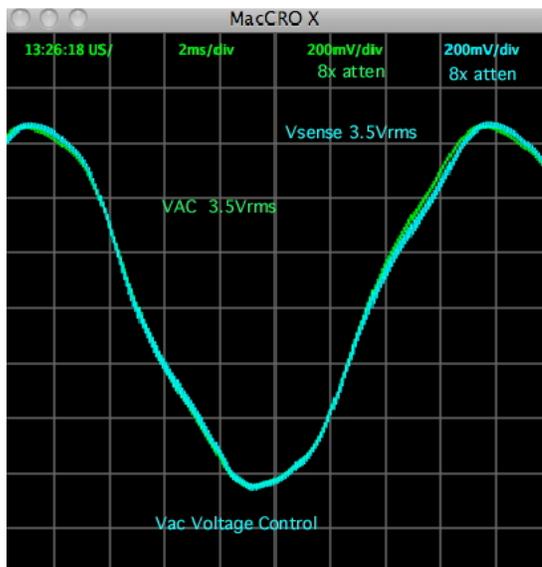


The bidirectional mode of operation involves monitoring the the **secondary's voltage** instead. In this case the secondary voltage times some constant **Kgain** is used to modulate the duty cycle.

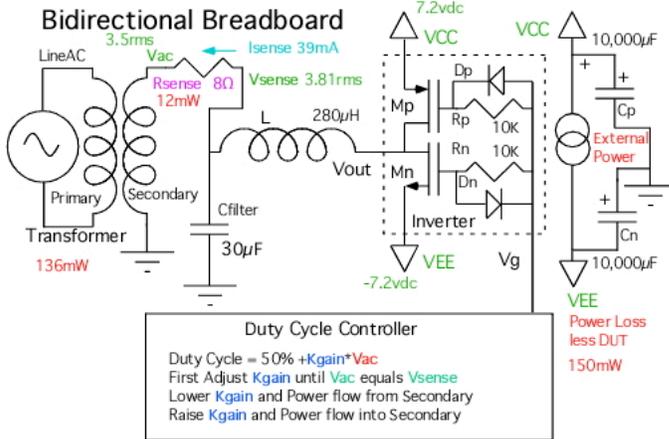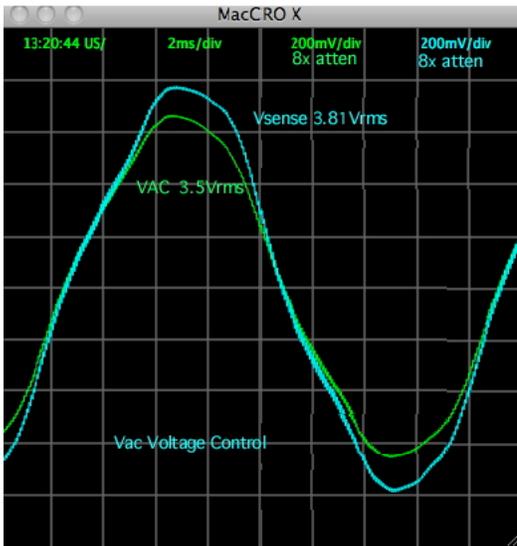There will be some value for **Kgain** where the **Vsense** voltage equals the **VAC** input voltage. Under this condition, little power should flow. The two AC waveforms off the breadboard are shown above. This should raise some questions as to how close can the duty cycle get to reflect the voltage that will appear at **Vsense**.




Now if this value for K_{gain} is increased, then the v_{sense} voltage can get larger than V_{ac} , and now power is flowing into the 60Hz AC socket. Unlike normal AC inverters, this is transferring power from the split supplies as a **negative resistor**. The waveforms above show that V_{sense} is larger than V_{ac} . An external power source needs to be applied to VCC and VEE to do this test. It appears that the power drain on the external supply is what would be expected.

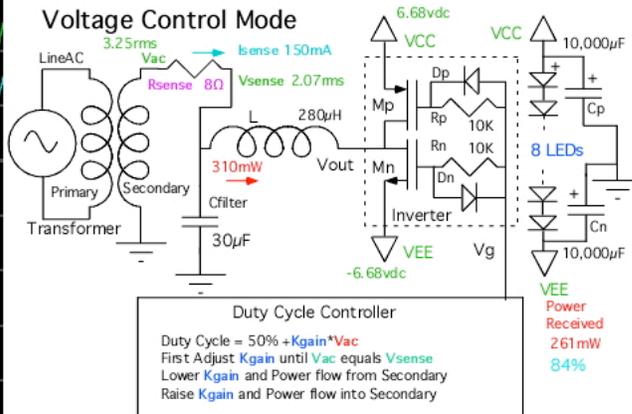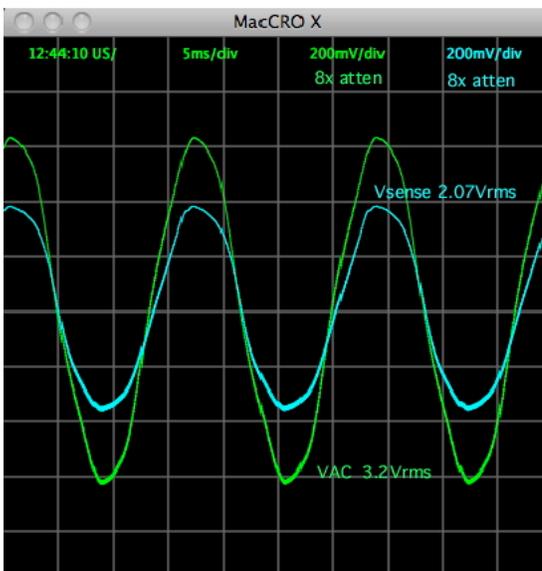


Lower the value of K_{gain} enough, and now the power is flowing from AC to DC. This method of voltage driving the duty cycle mode appears to be ideal for bidirectional AC \leftrightarrow DC power transfer since the circuit goes to an open circuit between the power flow directions.

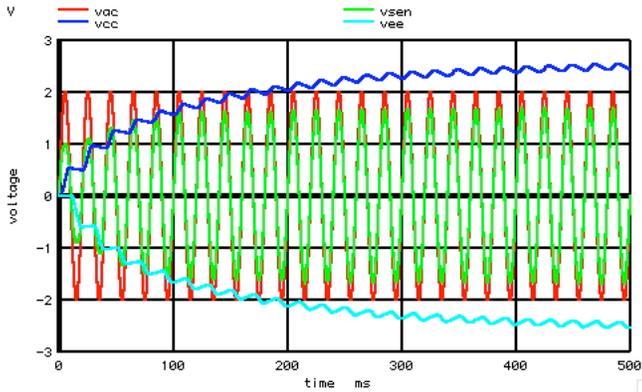In this breadboard, the efficiency appears to be around 84%. It is not obvious how this invention is little more than just using a simple DC to DC converter in a new application. If that is so, then the same efficiencies for DC to DC converters should be possible.



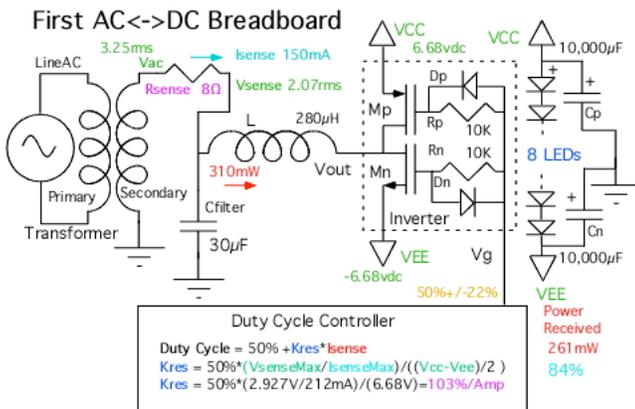This breadboard is actually self starting. When the AC first turns on, it forward biases the drain bulk junctions of both power MOSFETs. This turns on the duty cycle controller which drives the split supplies to a level higher than the AC input voltage.



When the breadboard is doing the job of a full wave rectifier, it loads the AC line exactly like a resistor. According to some recent articles in EDN and Power Electronics Technology, things like having a high power factor is becoming important.

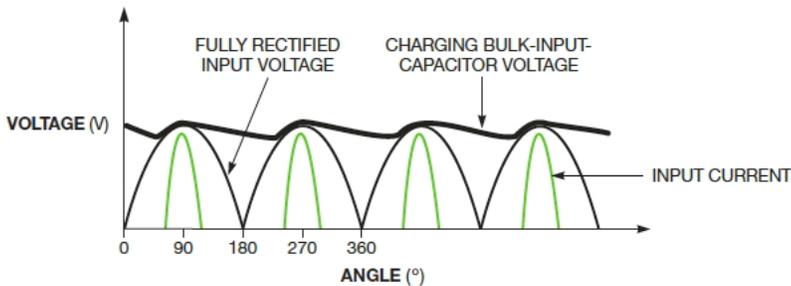


Figure 2 Superimposing the current over the voltage for the circuit in Figure 1 shows the need for a PFC to shape the current.

Apparently the nonlinear loading of full wave rectifier circuits is starting to create a need to raise the power factor of AC to DC converters.

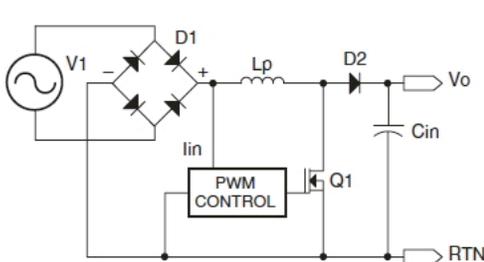


Figure 8. PFC Boost Pre-Regulator


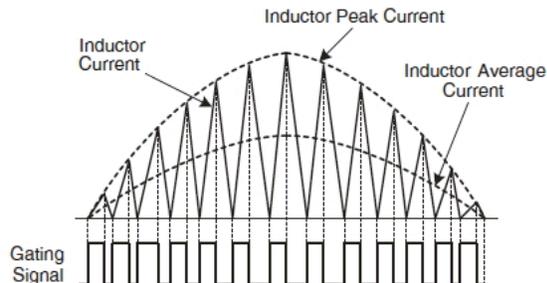
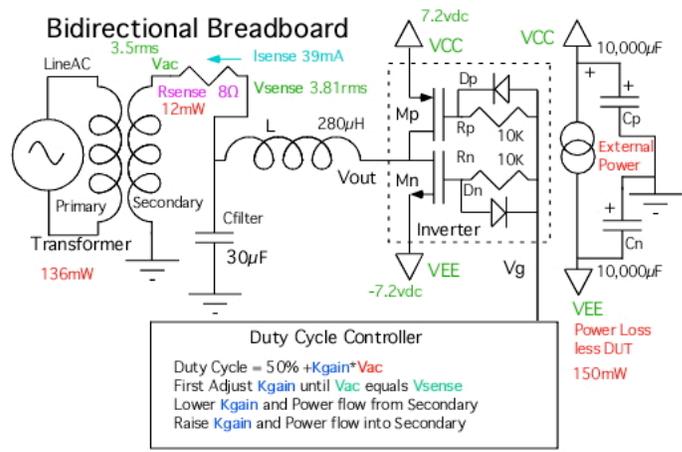



Figure 9. Discontinuous mode of operation

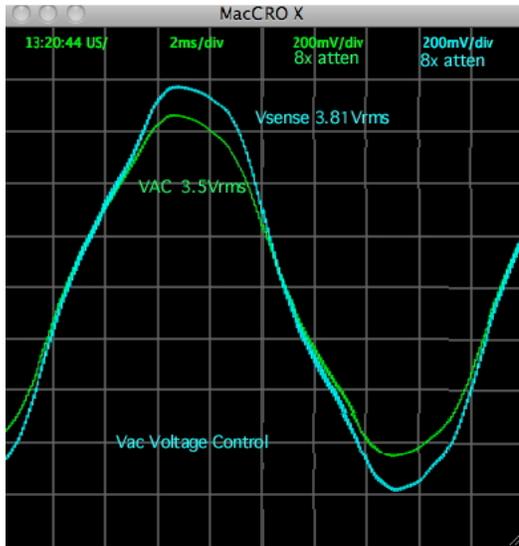The figures above are from a [Fairchild application Note](#) about Power factor correction. The attempt is to be able to draw power off the ac line like a resistor. Not very many power factor reduction methods however lack rectifiers in the power signal path.



The breadboard sure does look like it can load the ac line like a linear resistor. And even as a negative linear resistor. If solar power becomes more widespread, would it generate a need for a high power factor DC to AC convertor?


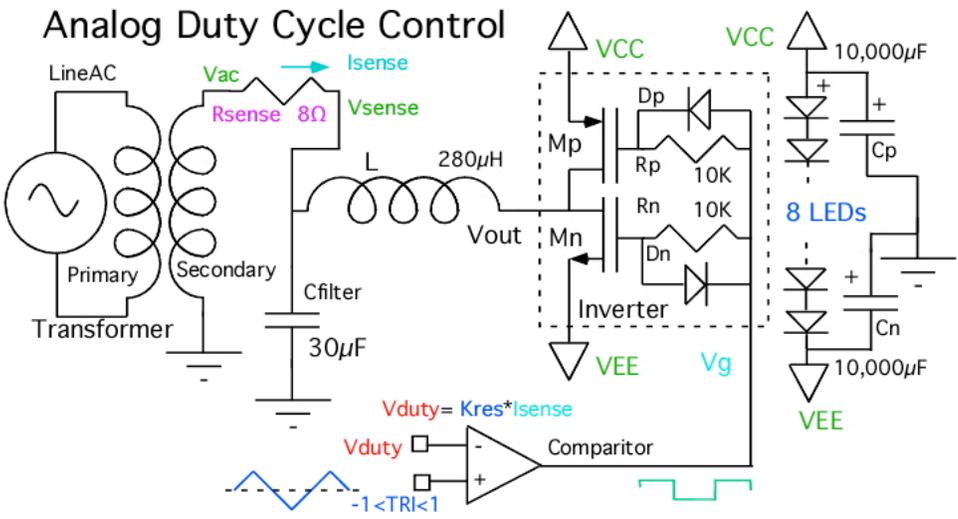
The power companies are installing smart meters in peoples homes. This might allow power companies to charge customers at different rates over the day. Could it be economical someday to store AC power into home batteries during the time when rates are low, and then reconvert it back to AC for use when rates are high?



The invention is mainly just a DC to DC converter with differences in terms of input/output ports, and in how the duty/cycle gets defined. The easy way to do the duty cycle in analog is to build up a triangle waveform, and stick it into one input of a voltage comparator. An analog signal voltage on the other input will modulate the duty cycle.

The analog signal and its effect on the duty cycle is doing two things. First it generates a voltage at Vsense which is scaled between the two supply voltages. Second, the duty cycle multiplexes any current through the sense resistor between the two power MOSFETs and their power supplies.


System Model

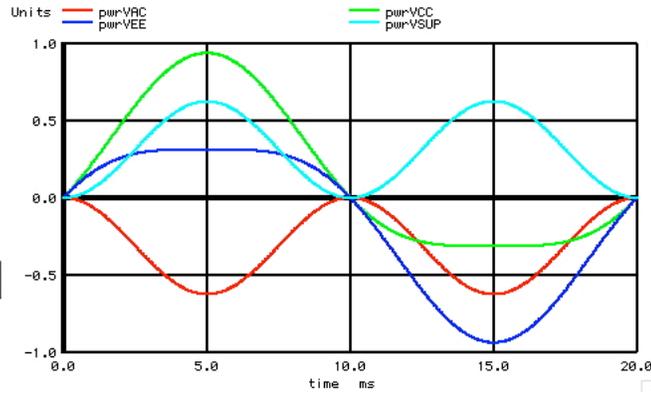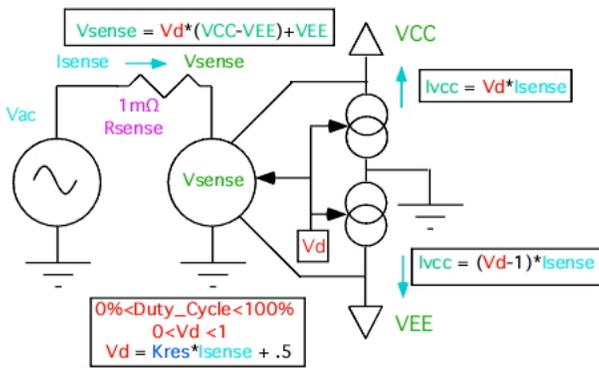

The system model above can show all the equations. For this system model, the analog voltage V_d is being defined to go from 0 to 1, which corresponds to a 0 to 100% duty cycle. This duty cycle V_d is being modulated by the I_{sense} current at some gain. The V_d voltage will both define the voltage V_{sense} , and will multiplex any I_{sense} current. Consider what happens when V_{ac} and V_{sense} are identical. No I_{sense} current will flow, and zero current will get multiplexed between the two MOSFETs.

Because the V_d term, which defines the V_{sense} voltage, is being scale by the input current, the V_{ac} voltage source will see a load looking like a linear resistor. Now the current multiplexing will always be charging up one of the supplies and discharging the other. But when the total power of both supplies are summed together, they are receiving close to the same power that the V_{ac} source is being loaded with. Naturally any IR drop in the power path will reduce efficiency.

Power Regulation

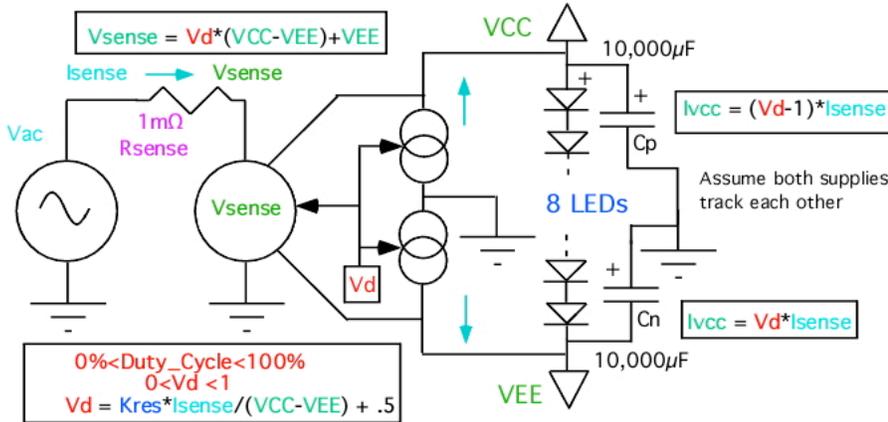


This invention tends to have a native output format of power regulation. For instance, if the output loads are LEDs, and if the voltage across LEDs can drift with temperature, the output current will auto-adjust itself to maintain the same output power.


For the sake of tying up any loose ends, one might be inclined to make the V_d value track the inverse of the supply voltages. Since the V_{sense} voltage is being scaled by the supply voltages, that means the V_{sense} magnitude should be insensitive to the supply voltages. If so, then the same input I_{sense} produces the same V_{sense} . So the simulated load resistance across V_{ac} will not change. So the power transfer will be independent of the split supplies voltages.

Suppose both VEE and VCC increase by 10%. The same I_{sense} current should produce a V_d with a 10% decrease in modulation. But the V_{sense} is also scaled by the 10% higher VCC and VEE voltages. So V_{sense} comes out the same. But the multiplexing of I_{sense} current has been reduced by 10%. So the two supplies are at a 10% higher voltage, but they are receiving 10% less charging up current.


Voltage Regulation

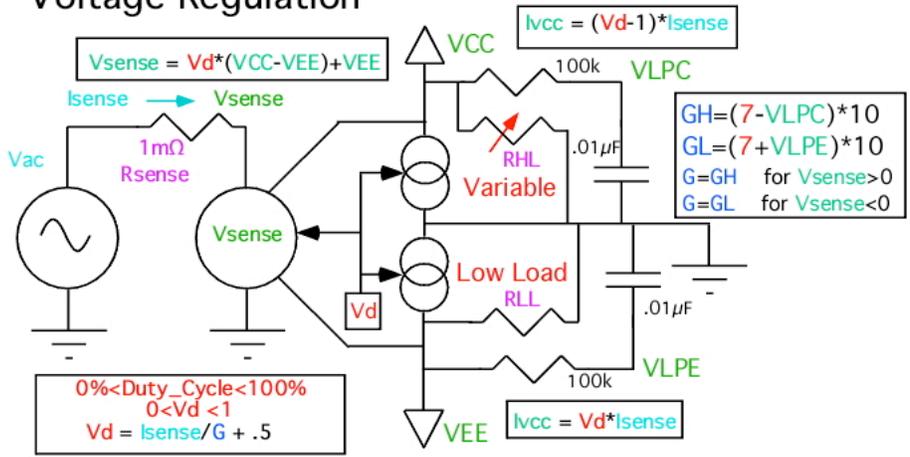

Now normally the output power is formatted in a voltage regulated mode. There is nothing stopping the voltage to current relationship to the input resistor from being adjusted in terms of both magnitude or asymmetry. Because V_{CC} gets charged up when V_{ac} is positive, and V_{EE} when negative, it is possible to regulate both V_{CC} and V_{EE} independently. The system simulation above shows both V_{CC} and V_{EE} being regulated to 7 volts. The supply voltages are low pass filtered since feedback should have a one pole compensation. The loop gain is set to 10. Different values for G get switched in depending on V_{ac} polarity.

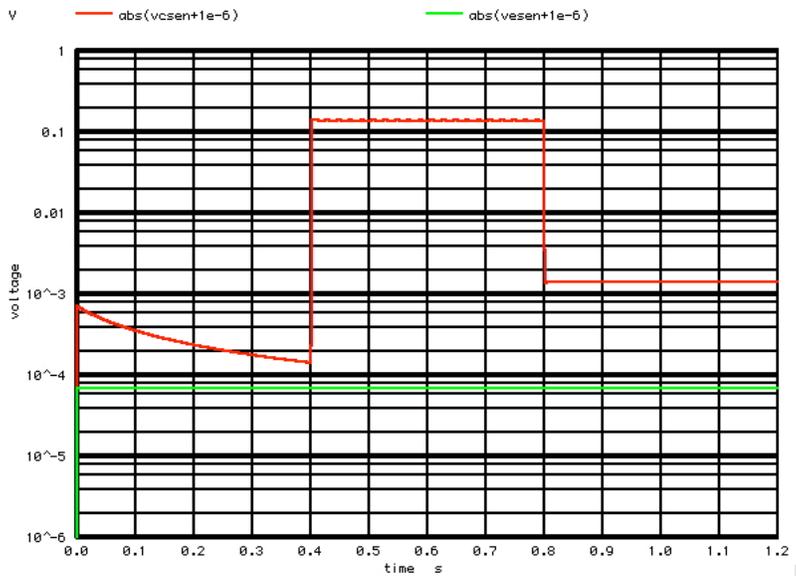


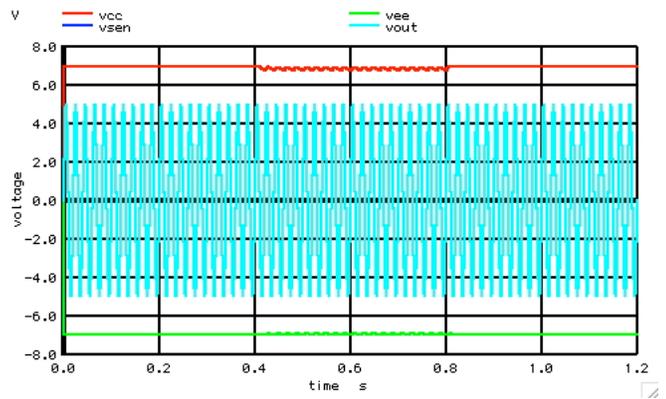In this example, V_{EE} will lightly load with constant 50uA load. But V_{CC} will vary its load in steps over three orders of magnitude.



Under heavy load, one would expect V_{CC} to develop some ripple. But V_{EE} appears to develop ripple at the same time. This is

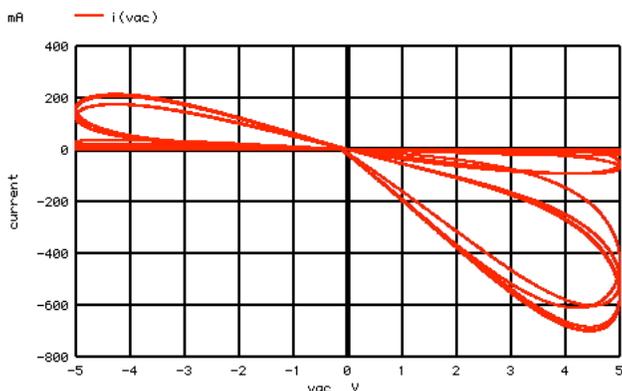
due to the fact that whenever VCC is being charged, VEE is being discharged. The VEE feedback loop needs to recover this lost charge when Vac is negative. So even when VCC is the only supply being used, the Vac voltage can not be completely asymmetrically loaded.



The asymmetry of the current loading on the AC line is shown above. So this type of AC to DC converter cannot load the AC line like a one diode rectifier. The lowpass filtering is not at the moment low enough to reduce the looping in the current loading curve. These low pass filters will affect the voltage regulation response to load current spikes. The step response to a high load current appears to be fast attack, slow decay.

For single supply applications, it may make more sense to build up a second DC switching network as is shown on [figure 9 on this web page](#) to transfer charge from one supply to the next. This enables the resistive loading to be symmetrical.

First Working Breadboard

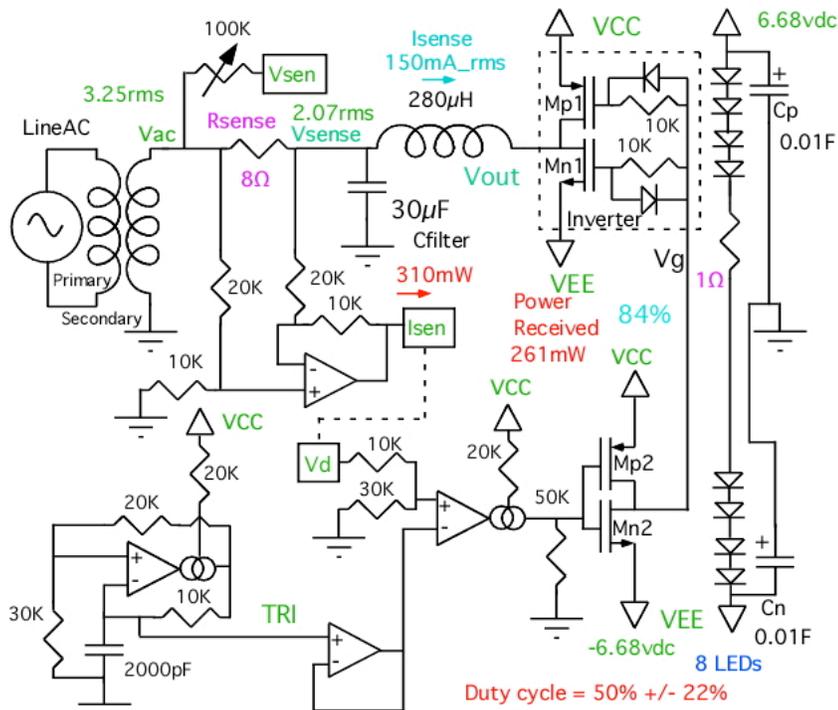

The full circuit for the breadboard is above. A secondary sense current node and secondary voltage sense node are provided, and both have been checked out. A LM13600 is being used to provide an easily scaleable triangle wave, and it is also used as a voltage comparator. A LM6144 is being used to buffer the triangle wave, and to measure the current through the 8 Ohm sense resistor. A CD4007 is being used to drive the Power MOSFETS. These MOSFETS have large capacitances, and adding some diodes and resistors appear to reduce the shoot through current.

Most of the supply current is going to the LM13600. It draws in fact

a little too much supply current. It is mainly being used just to check out some scaling concepts. The duty cycle controller mainly needs just a triangle wave source and a comparator. The gate resistor/diodes networks certainly could be replaced with something better in order to operate at higher frequencies. The sense resistor is set at 8 ohms in order to make the voltage across it obvious enough to show things like bidirectional power flow. The Triangle wave is running below 20KHz, so the 30uF cap (two 60uF electrolytics) is chosen just to make the Vsense signal look clean.

Other breadboard experiments are in the works. Running spice simulations side by side with a working breadboard has some crosschecking advantages. Some of the components used to build the AC<->DC converter hardware are shown below.



There appears to be a lot of recent patent activity in the area of building "bridgeless PFC convertors". The following are some of the patents.

- [11 584 983 Method and apparatus for high efficiency rectifier](#)
- [11 204 307 AC to DC power supply with PF](#)
- [11 302 544 Simple partial switching power factor correction](#)
- [11 474 712 BRIDGELESS BI DIRECTIONAL FORWARD TYPE CONVERTER](#)
- [11 480 004 High efficiency power converter system](#)
- [11 706 645 AC to DC voltage converter as power supply](#)
- [12 401 983 BRIDGELESS PFC CIRCUIT FOR CRM](#)
- [12 798 682 Bridgeless PFC converter](#)

- [3295043 MASSEY D C TO D C REGULATED CONVERTER](#)
- [4183079 DC AC inverter](#)
- [4523266 AC to DC conversion system](#)
- [4943902 AC to DC power converter and method](#)
- [5570276 Switching converter with open loop input regulation](#)
- [5815380 Switching converter with open loop Primary regulation](#)
- [5815384 Transformer uses bi directional synch Rectifiers](#)
- [6115267 AC DC converter with no input rectifiers](#)
- [6157182 DC DC converter with multiple operating modes](#)
- [6608522 DC to DC converter providing stable operation](#)
- [7250742 Digital control of bridgeless power factor correction](#)
- [7265591 CMOS driver with minimum shoot through](#)

And here is some more information for those who may be interested.

- [A BIDIRECTIONAL PWM THREE-PHASE STEP-DOWN RECTIFIER](#)
- [A bidirectional, sinusoidal, high-frequency inverter](#)
- [A DUAL INPUT BIDIRECTIONAL POWER CONVERTER](#)
- [A new structure for bidirectional Power flow](#)
- [BI-DIRECTIONAL INVERTER-CHARGER](#)
- [Bi-directional single-phase half-bridge rectifier for power quality](#)
- [BiDirectional Converter](#)

Bidirectional_UP_Inverter
Synthesis of Input-Rectifierless AC/DC

11.28.10_10.11AM
dsauersanjose@aol.com
Don Sauer
<http://www.idea2ic.com/>