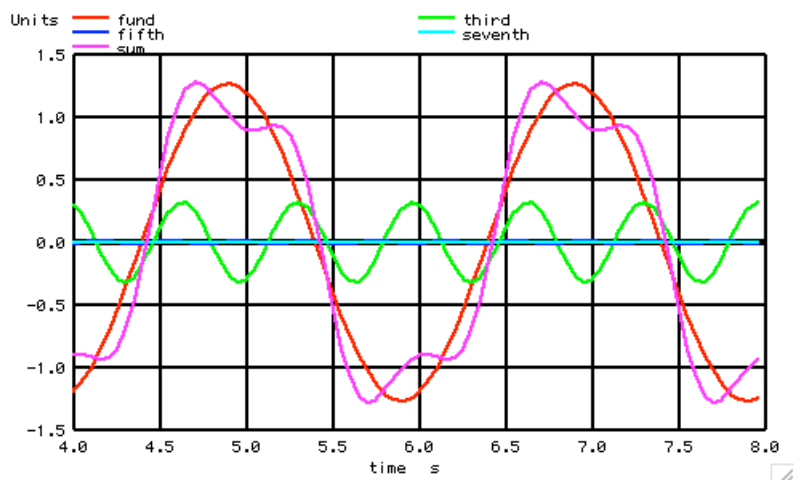


# \*====Better\_Butterworth\_GroupDelay====


RUN A SQUARE WAVE THROUGH A 6 POLE BUTTERWORTH.  
 EXTRACT ALL THE OUTPUT HARMONICS.  
 RECONSTRUCT THE OUTPUT WAVEFORM FROM THE HARMONICS.  
 VIEW THE DELAY OF ALL THE HARMONICS.  
 AND DO SO IN ONE SPICE FILE.



The dissection of the harmonics of a lowpass filter's output can show how phase delay effects group delay.

Below is a behavioral model for a 6 pole Butterworth filter.
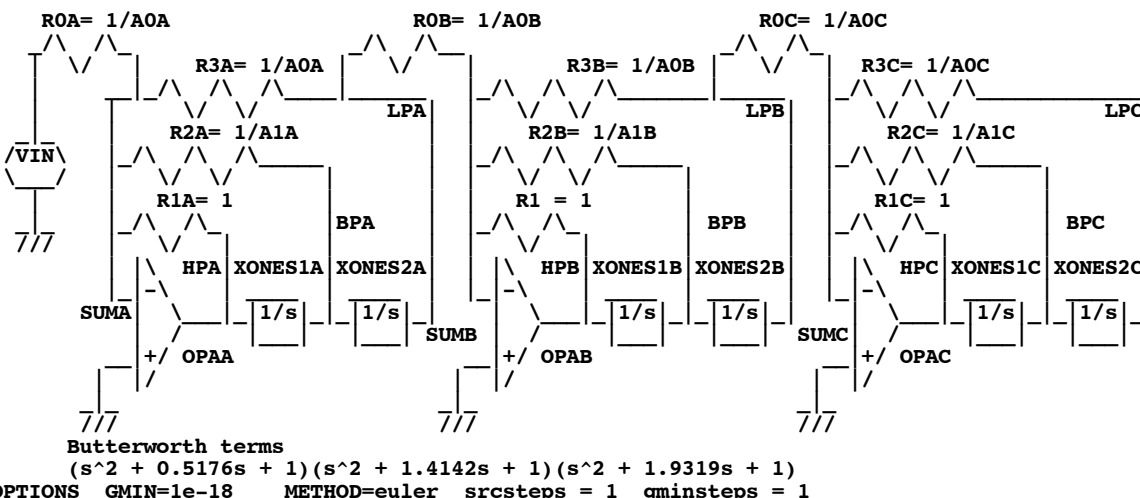
```
=====
Better_Butterworth_6P_State_Variable
* dsauersanjose@aol.com
* www.idea2ic.com
* 8.13.10_10.02AM
*
```



## \*====Using\_Simple\_Amplifiers====

Pretty idealized models are being used for Op Amps and integrators.

```
=====
*V PULSE# NODE_P NODE_N DC VALUE PULSE( VINIT VPULSE TDELAY TRISE TFALL PWIDTH PERIOD )
V_IN VIN 0 DC 0 PULSE( -1 1 100u 100u 100u 1 2 ) AC = 1
ROA VIN SUMA 1
R1A SUMA HPA 1

```

```


R2A      SUMA  BPA  1.9319
R3A      SUMA  LPA  1
BOPA1A   HPA  0      V =   5*tanh(tanh((-v(SUMA))*100)*100)
XONES1A  HPA  BPA  ONE_S
XONES2A  BPA  LPA  ONE_S
ROB      LPA  SUMB  1
R1B      SUMB  HPB  1
R2B      SUMB  BPB  .707
R3B      SUMB  LPB  1
BOPA1B   HPB  0      V =   5*tanh(tanh((-v(SUMB))*100)*100)
XONES1B  HPB  BPB  ONE_S
XONES2B  BPB  LPB  ONE_S
R0C      LPB  SUMC  1
R1C      SUMC  HPC  1
R2C      SUMC  BPC  .5176
R3C      SUMC  LPC  1
BOPA1C   HPC  0      V =   5*tanh(tanh((-v(SUMC))*100)*100)
XONES1C  HPC  BPC  ONE_S
XONES2C  BPC  LPC  ONE_S
Binv     LPD  0      V =   -V(LPC)

```

```

*=====Integrator_Cell=====

```

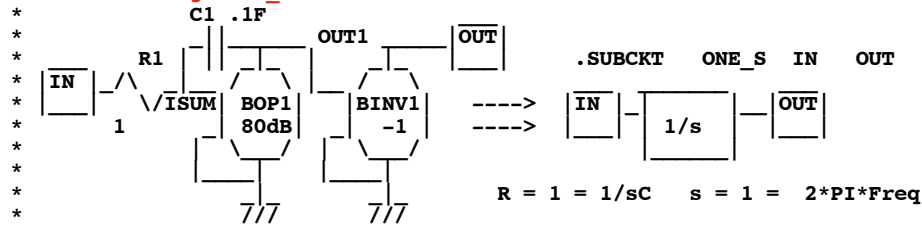

```

.SUBCKT  ONE_S  IN  OUT
R1      IN      ISUM  1
C1      ISUM    OUT1  .1
BOP1    OUT1    0      V =   5*tanh(tanh((-v(ISUM))*100)*100)
BINV1   OUT     0      V =   -v(OUT1)
.ends

```

```

*=====Simple Simulations=====

```


It is not hard to do **AC** and **Transient** tests.


```

=====  

.control
ac      dec    500  .01  100
plot    db(lpc)
*TRAN   TSTEP  TSTOP  TSTART  TMAX
tran    50m    7.95  4      50m

```

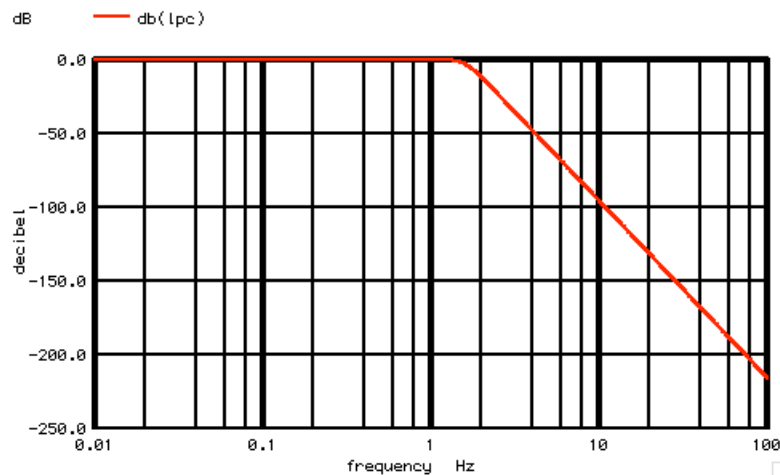

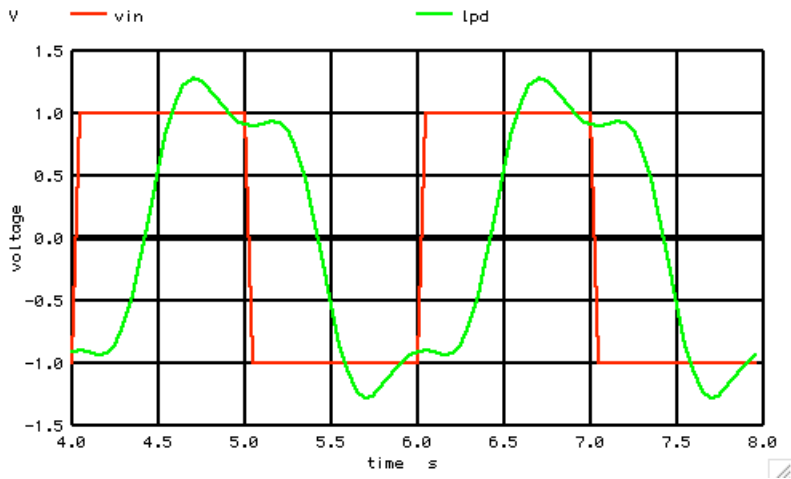


The AC test shows that the frequency roll off is pretty sharp.

But look at how the output of the low pass filter rings. Looking at what happened to all the harmonics to the input square wave can show what happened.

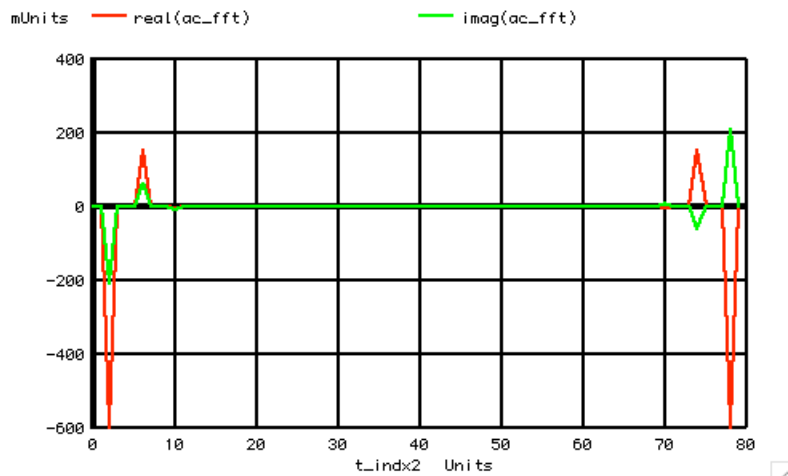**\*=====Look\_at\_the\_Output\_Spectrum=====**

The FFT reveals that only the fundamental and third harmonic got through the lowpass filter.

```
linearize
plot      vin      lpd
let      numb2    = length(vin)
print    numb2
let      t_indx2  = vector($&numb2)
let      ac       = lpd +j(0)
let      ac_fft   = fft(ac)
plot     real(ac_fft) imag(ac_fft) vs t_indx2
```



**\*=====The\_Harmonics\_Can\_Be\_Dissected=====**

The dissection of the harmonics show the results


```
let      funbin   = 2
let      unvect   = unitvec($&numb2)
```

```

let      fundspec          = unvect*0 +j(0)
let      fundspec[2]      = real(ac_fft[2])      +j(imag(ac_fft[2] ))
let      fundspec[numb2-2] = real(ac_fft[numb2-2]) +j(imag(ac_fft[numb2-2] ))
let      fund             = ifft(fundspec)
let      thirdspect      = unvect*0 +j(0)
let      thirdspect[6]   = real(ac_fft[6])      +j(imag(ac_fft[6] ))
let      thirdspect[numb2-6] = real(ac_fft[numb2-6]) +j(imag(ac_fft[numb2-6] ))
let      third           = ifft(thirdspect)
let      fiftspect       = unvect*0 +j(0)
let      fiftspect[10]   = real(ac_fft[10])     +j(imag(ac_fft[10] ))
let      fiftspect[numb2-10] = real(ac_fft[numb2-10]) +j(imag(ac_fft[numb2-10] ))
let      fifth          = ifft(fiftspect)
let      seventspect     = unvect*0 +j(0)
let      seventspect[14] = real(ac_fft[14])     +j(imag(ac_fft[14] ))
let      seventspect[numb2-14] = real(ac_fft[numb2-14]) +j(imag(ac_fft[numb2-14] ))
let      seventh        = ifft(seventspect)
let      sum = fund + third + fifth + seventh
set      scale time
plot     fund third fifth seventh sum

```

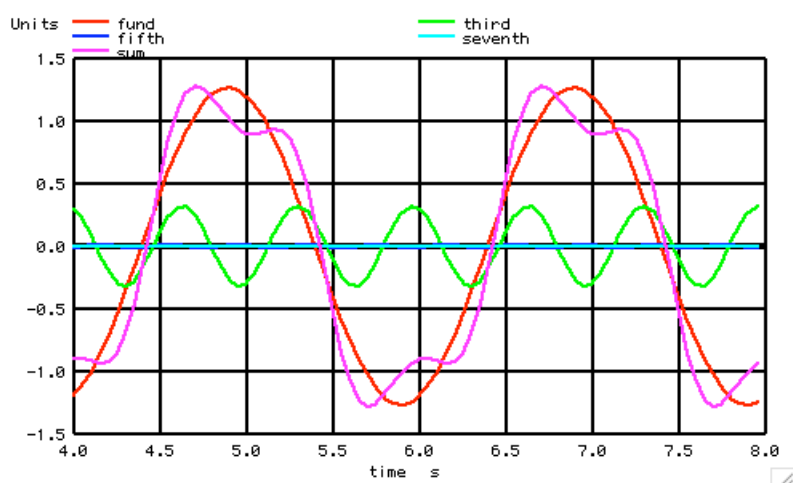plot fund third fifth seventh sum xlimit 5.2 5.7  
.endc



Notice that the output is just fundamental and third. But also notice that the zero crossings are not the same. In other-words, fundamental and third don't have the same time delay.


**\*=====Now\_Look\_At\_Harmonic\_Delays=====**

Here is a better view of the different time delays. This square wave is looking like it has been put through a RC filter.

```

=====
plot     fund third fifth seventh sum xlimit 5.2 5.7
.endc


```

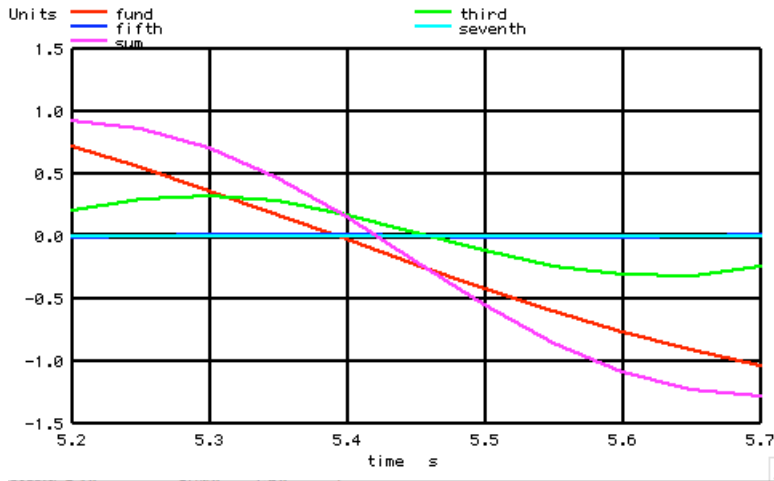

=====**Full Netlist For Copy\_Paste**=====

Better\_Butterworth\_6P\_State\_Variable

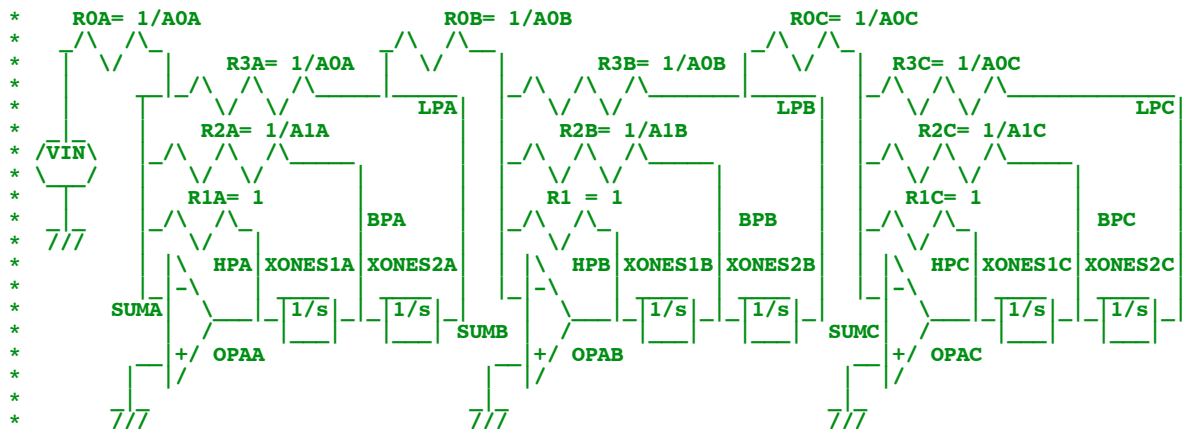\* dsauersanjose@aol.com  
 \* www.idea2ic.com  
 \* 8.13.10\_10.02AM  
 \*



Butterworth terms


$$(s^2 + 0.5176s + 1)(s^2 + 1.4142s + 1)(s^2 + 1.9319s + 1)$$

.OPTIONS GMIN=1e-18 METHOD=euler srcsteps = 1 gminsteps = 1

*V_PULSE#	NODE_P	NODE_N	DC	VALUE	PULSE(	VINIT	VPULSE	TDELAY	TRISE	TFALL	PWIDTH	PERIOD )
V_IN	VIN	0	DC	0	PULSE(	-1	1	100u	100u	100u	1	2 ) AC = 1
ROA	VIN	SUMA	1									
R1A	SUMA	HPA	1									
R2A	SUMA	BPA	1.9319									
R3A	SUMA	LPA	1									
BOPA1A	HPA	0	V =	5*tanh(tanh((-v(SUMA))*100)*100)								
XONES1A	HPA	BPA	ONE_S									
XONES2A	BPA	LPA	ONE_S									
ROB	LPA	SUMB	1									
R1B	SUMB	HPB	1									
R2B	SUMB	BPB	.707									
R3B	SUMB	LPB	1									
BOPA1B	HPB	0	V =	5*tanh(tanh((-v(SUMB))*100)*100)								
XONES1B	HPB	BPB	ONE_S									
XONES2B	BPB	LPB	ONE_S									
ROC	LPB	SUMC	1									
R1C	SUMC	HPC	1									
R2C	SUMC	BPC	.5176									
R3C	SUMC	LPC	1									
BOPA1C	HPC	0	V =	5*tanh(tanh((-v(SUMC))*100)*100)								
XONES1C	HPC	BPC	ONE_S									
XONES2C	BPC	LPC	ONE_S									
Binv	LPD	0	V =	-V(LPC)								

\*=====Integrator\_Cell=====

\* C1 .1F

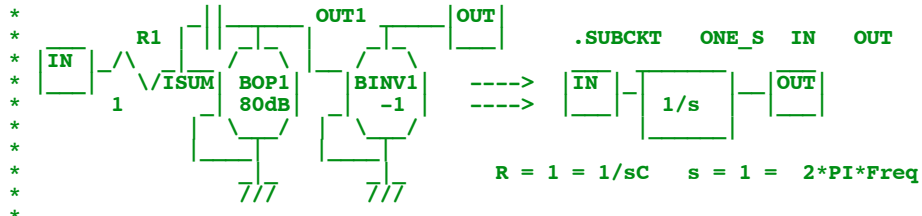

```

.SUBCKT ONE_S IN OUT
R1 IN ISUM 1
C1 ISUM OUT1 .1
BOP1 OUT1 0 V = 5*tanh(tanh((-v(ISUM))*100)*100)
BINV1 OUT 0 V = -v(OUT1)
.ENDS

```

\*\*\*\*\*A\_Bessel\_is\_Best\_for\_Low\_Phase\_Distortion\*\*\*\*\*

```

.control
ac dec 500 .01 100
plot db(lpc)
*TRAN TSTEP TSTOP TSTART TMAX
tran 50m 7.95 4 50m

```

```

linearize
plot vin lpd
let numb2 = length(vin)
print numb2
let t_indx2 = vector($&numb2)
let ac = lpd + j(0)
let ac_fft = fft(ac)
plot real(ac_fft) imag(ac_fft) vs t_indx2

let funbin = 2
let unvect = unitvec($&numb2)
let fundspec = unvect*0 + j(0)
let fundspec[2] = real(ac_fft[2]) + j(imag(ac_fft[2] ))
let fundspec[numb2-2] = real(ac_fft[numb2-2]) + j(imag(ac_fft[numb2-2] ))
let fund = ifft(fundspec)
let thirdspect = unvect*0 + j(0)
let thirdspect[6] = real(ac_fft[6]) + j(imag(ac_fft[6] ))
let thirdspect[numb2-6] = real(ac_fft[numb2-6]) + j(imag(ac_fft[numb2-6] ))
let third = ifft(thirdspect)
let fiftspect = unvect*0 + j(0)
let fiftspect[10] = real(ac_fft[10]) + j(imag(ac_fft[10] ))
let fiftspect[numb2-10] = real(ac_fft[numb2-10]) + j(imag(ac_fft[numb2-10] ))
let fifth = ifft(fiftspect)
let seventhspect = unvect*0 + j(0)
let seventhspect[14] = real(ac_fft[14]) + j(imag(ac_fft[14] ))
let seventhspect[numb2-14] = real(ac_fft[numb2-14]) + j(imag(ac_fft[numb2-14] ))
let seventh = ifft(seventhspect)
let sum = fund + third + fifth + seventh
set scale time
plot fund third fifth seventh sum

plot fund third fifth seventh sum xlimit 5.2 5.7
.endc

```

.end