
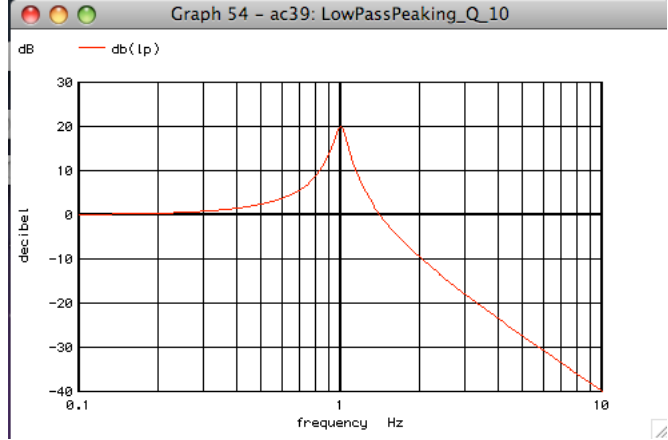


=====LC Simple Q=====

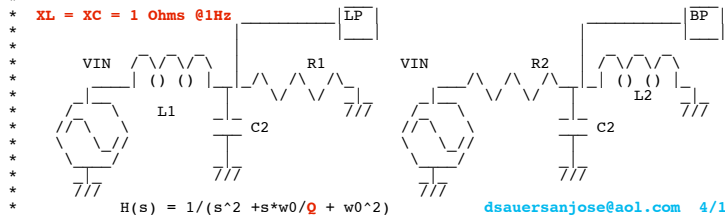

Simple_Q

* http://www.idea2ic.com/PlayWithJavascript/L_C_R_F.html



```
.OPTIONS GMIN=1e-15 METHOD=gear ABSTOL=1e-15 TEMP=27 srcsteps = 1 gminsteps = 1
VIN      0      DC 0V
L1       VIN    LP  .159
C1       LP     0    .159
R1     LP     0    10
R2     VIN    BP  10
L2       BP     0    .159
C2       BP     0    .159
```

*=====Q Or Quality Factor Tells A Lot=====

.control

*#1=====Q is the Number Of Cycles To Settle Out=====

```
tran      1      20      0
run
plot      lp      title Settle_Time_Q_10
```

*#2=====Q Also Defines A Lowpass Filters Peaking=====

```
ac        dec    200    .1    10
run
plot      db(lp)  title LowPassPeaking_Q_10
```

*#3=====Q Also Defines the Bandwidth Of A BandPass=====

```
plot      db(bp)  linear ylimit -3 0 xlimit .9 1.1 title BandPassBW_Q_10
```

```

*#4=====Q_is_Reduced_From_10_to_1_to_Show_the_Effects=====
alter      R1      resistance  =  1
alter      R2      resistance  =  1

tran       1       20       0
run
plot       lp       title  Settle_Time_Q_1
*#6=====Q_is_Reduced_From_10_to_1_to_Show_the_Effects=====
ac         dec      200      .1      10
run
plot       db(lp)   title  LowPassPeaking_Q_1
*#7=====Q_is_Reduced_From_10_to_1_to_Show_the_Effects=====
plot       db(bp)   linear  ylimit -3 0 xlimit .1 2 title BandPassBW_Q_1
.endc
.end

```

=====END_OF_SPICE=====

```

#1=====Q_is_the_Number_Of_Cycles_To_Settle_Out=====


```

```

tran       1       20       0
run
plot       lp       title  Settle_Time_Q_10

```

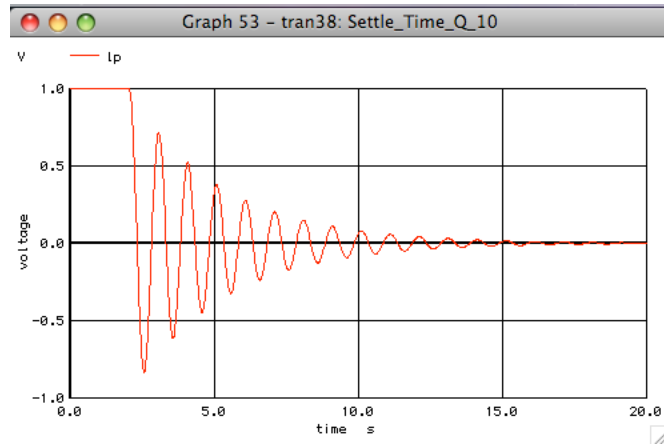The settle time for Q=10 is about 10 cycles



```

*#2=====Q_Also_Defines_A_Lowpass_Filters_Peaking=====


```

```

ac         dec      200      .1      10
run
plot       db(lp)   title  LowPassPeaking_Q_10

```

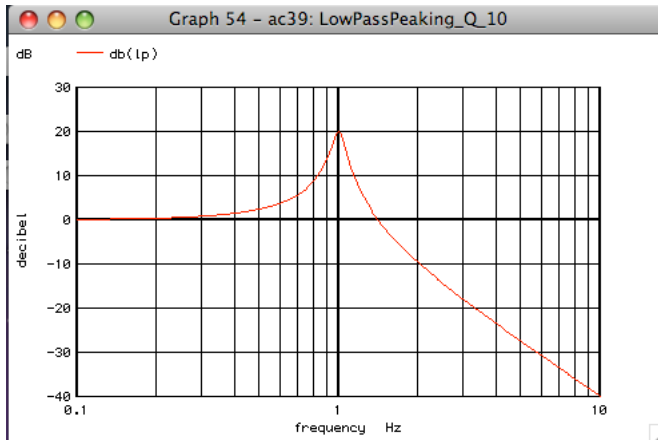The lowpass peaking for Q=10 is about a factor of 10




```

*#3=====Q_Also_Defines_the_Bandwidth_of_A_BandPass=====
plot      db(bp)  linear ylimit -3 0 xlimit .9 1.1 title BandPassBW_Q_10

```

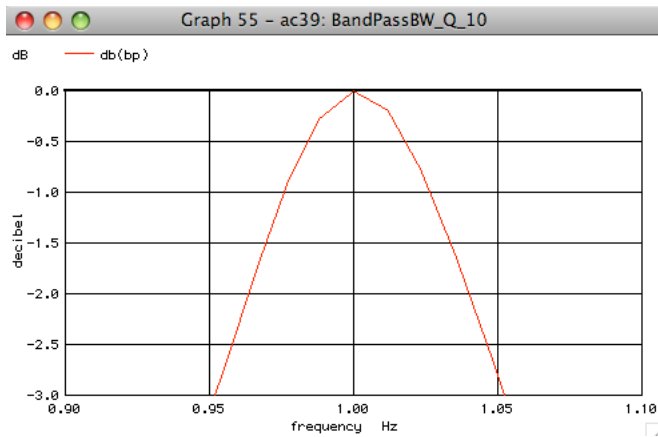The bandwidth for Q=10 is 1/10th center freq



```

*#4=====Q_is_Reduced_From_10_to_1_to_Show_the_Effects=====

```

```


alter     R1    resistance = 1
alter     R2    resistance = 1

tran      1      20      0
run
plot      1p    title  Settle_Time_Q_1

```

The settle time for Q=1 is about 1 cycles

Graph 94 - tran305: Settle_Time_Q_1

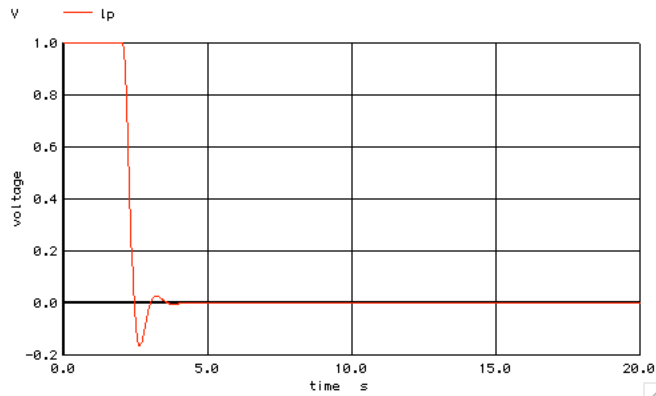


***#6=====Q is Reduced From 10 to 1 to Show the Effects=====**

```
ac
run
plot      db(lp)    title LowPassPeaking_Q_1
```

The lowpass peaking for Q=1 is about a factor of 1

Graph 95 - ac306: LowPassPeaking_Q_1

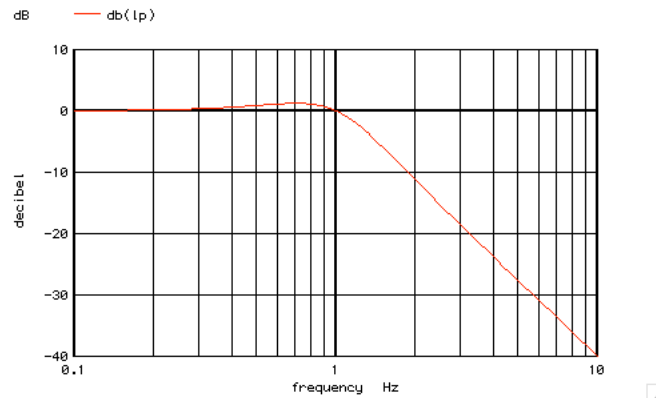

***#7=====Q is Reduced From 10 to 1 to Show the Effects=====**

```
plot      db(bp)    linear ylimit -3 0 xlimit .1 2 title BandPassBW_Q_1
```

The bandwidth for Q=1 is about center freq

Graph 96 - ac306: BandPassBW_Q_1

